

Chapter 6: Synchronous Sequential Circuits

Do Duy Tan, Ph.D

Synchronous sequential circuit

- Combinational logic circuits: The outputs are determined fully by the **present values of inputs**
- Flip-flop: The output depends on **the state of the flip-flop** rather than the value of its inputs at any given time; the **inputs cause changes in the state**
- Sequential circuit: The outputs depend on **the past behavior of the circuit**, as well as on the **present values of inputs**
 - Synchronous sequential circuit: **clock** signal is used to **control** the operation of a sequential circuit
 - The alternative, in which no clock signal is used, is called an asynchronous sequential circuit

Synchronous sequential circuit

- A sequential circuit is a circuit with **memory**, which forms the internal state of the circuit.
- Unlike a combinational circuit, in which the output is a function of input only, the output of a sequential circuit is **a function of the input and the internal state**.
- **The synchronous design methodology is the most commonly used practice** in designing a sequential circuit. In this methodology, all storage elements are controlled (i.e., synchronized) by **a global clock signal** and the data is sampled and stored at the rising or falling edge of the clock signal

Review of Verilog assignment and procedure

Continuous Assignments

review

- Continuously assigns right side of expression to left side.
- Limited to basic Boolean and ? operators. For example a 2:1 mux:

- ? operator

assign D = (A == 1) ? B : C; // if A then D = B else D = C;

- Boolean operators

assign D = (B & A) | (C & ~A); // if A then D = B else D = C;

Procedural Assignments

- Executes a procedure allowing for more powerful constructs such as if-then-else and case statement.
- For example 2:1 mux:
 - if-else
if (A) D = B else D = C;
 - case
case(A)
1'b1 : D = B;
1'b0 : D = C;
endcase

This is obviously much easier to implement and read than Boolean expressions!!

Always Block

- An always block is an example of a procedure.
- The procedure executes a set of assignments when a defined set of inputs **change**.


2:1 mux Always Block

```
Module mux_2_1(a, b, out, sel);  
    input a, b, sel;  
    output out;
```

```
    reg out;  
    always @ (a or b or sel)  
    begin  
        if (sel) out = a;  
        else out = b;  
    end
```

```
endmodule
```
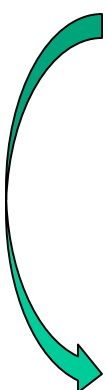
```
    wire out;  
    assign out =(sel==1)?a:b;
```



Declare Module and IO as before.

All data types in always blocks must be declared as a 'reg' type.

This is required even if the data type is for combinational logic.

The always block 'executes' whenever signals named in the sensitivity list change.

Literally: always execute at a or b or sel.

Sensitivity list should include conditional (sel) and right side (a, b) assignment variables.

As Easier Way to Implement the Sensitivity List


- Recent versions of Verilog provides a means to implement the sensitivity list without explicitly listing each potential variable.
- Instead of listing variables as in the previous example

always @ (a or b or sel)

Simply use

always @*

The * operator will automatically identify all sensitive variables.



Blocking vs Non-Blocking Assignments

- Blocking (=) and non-blocking (<=) assignments are provided to control the execution order within an always block.
- Blocking assignments **literally block** the execution of the next statement until the current statement is executed.
 - **Consequently, blocking assignments result in ordered statement execution.**

For example:

assume $a = b = 0$ initially;

$a = 1;$ //executed first

$b = a;$ //executed second

then $a = 1, b = 1$ after ordered execution

Blocking vs Non-Blocking Cont

- Non-blocking assignments **literally do not block** the execution of the next statements. The right side of all statements are determined first, then the left sides are assigned together.
 - **Consequently, non-blocking assignments result in simultaneous or parallel statement execution.**

For example:

assume $a = b = 0$ initially;


$\left. \begin{array}{l} a \leq 1; \\ b \leq a; \end{array} \right\}$ Execute together (in parallel)

then $a = 1, b = 0$ after parallel execution

Result is different from ordered exec!!! Does not preserve logic flow

To Block or Not to Block ?

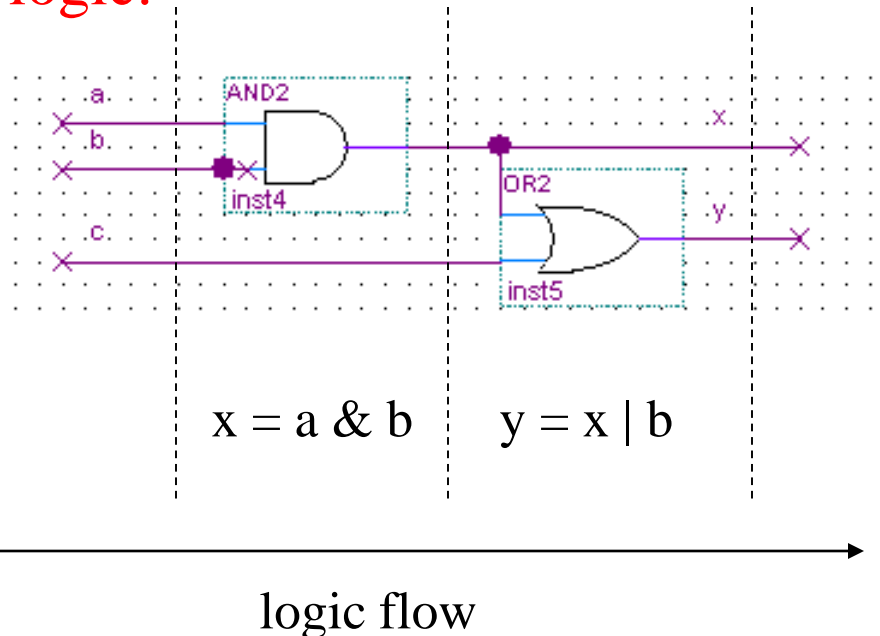- Ordered execution mimics the inherent logic flow of combinational logic.
- Hence blocking assignments (=) generally work better for combinational logic.
- For example:



To Block or Not to Block ? cont

Module blocking(a,b,c,x,y);

input a,b,c;

output x,y;

reg x,y;

always @*

begin

x = a & b;

y = x | c;

end

endmodule

Blocking behavior	a	b	c	x	y
Initial values	1	1	0	1	1
a changes → always block execs	0	1	0	1	1
x = a & b; //make assignment	0	1	0	0	1
y = x c; //make assignment	0	1	0	0	0

Module nonblocking(a,b,c,x,y);

input a,b,c;

output x,y;

reg x,y;

always @*

begin

x <= a & b;

y <= x | c;

end

endmodule

Non-blocking behavior	a	b	c	x	y
Initial values	1	1	0	1	1
a changes → always block execs	0	1	0	1	1
x = a & b;	0	1	0	1	1
y = x c; //x not passed from here	0	1	0	1	1
make x, y assignments	0	1	0	0	1

non-blocking behavior does not preserve logic flow!!

Synchronous sequential circuit

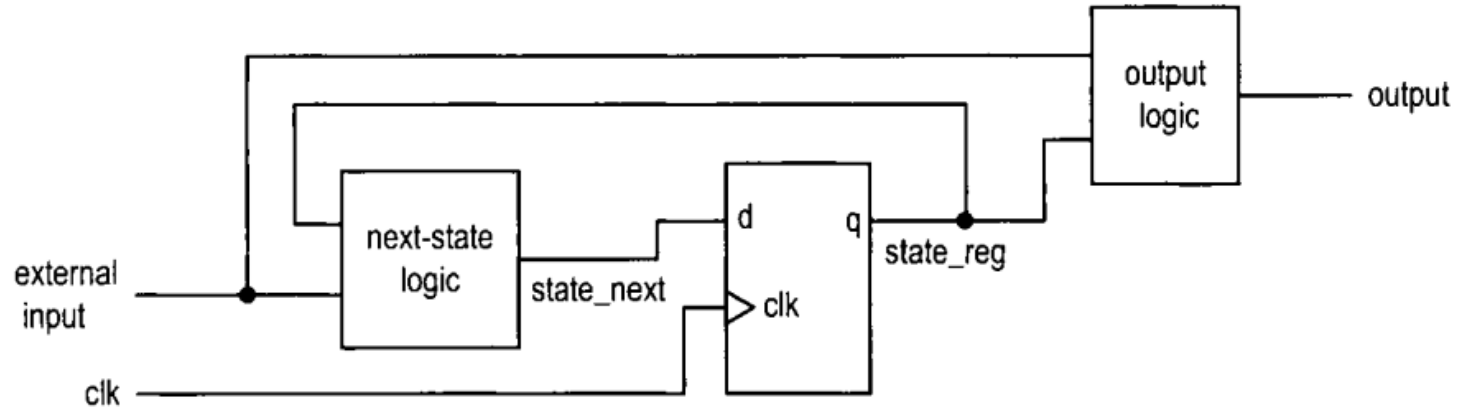



Figure 4.2 Block diagram of a synchronous system.

State register: a collection of D FFs controlled by the same clock signal


Next-state logic: combinational logic that uses the external input and internal state (i.e., the output of register) to determine the new value of the register

Output logic: combinational logic that generates the output signal

Design of synchronous counter

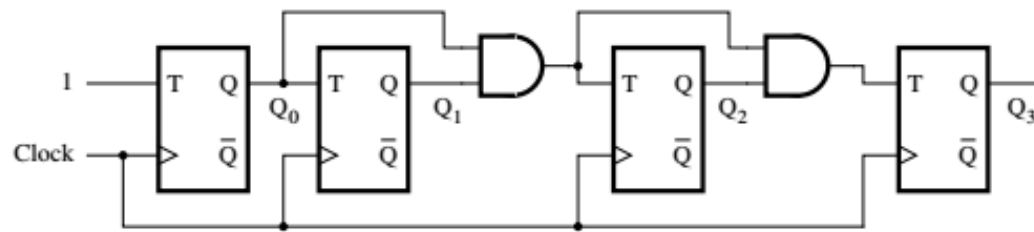

(a) Circuit

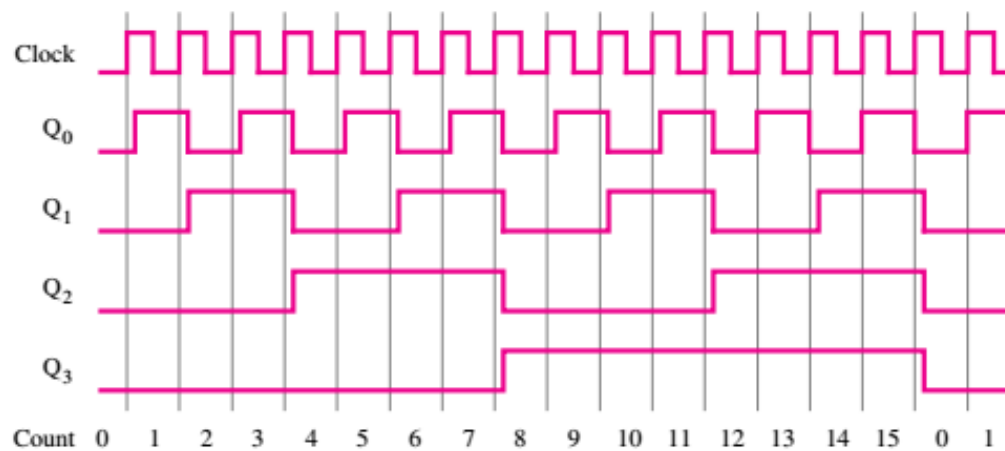

(b) Timing diagram

Figure 5.21 A four-bit synchronous up-counter.

Design of synchronous counter

```
module Counter
```

```
   #(parameter N= 8)
```

```
    ( input wire clk, reset,  
      output wire      [N-1:0] q );
```

```
    // signal declaration
```

```
    reg [N-1:0] r_reg;
```

```
    wire [N-1:0] r_next;
```

```
    // body, register
```

```
    always @(posedge clk, posedge reset)
```

```
    if (reset)
```

```
        r_reg <= 0;
```

```
    else
```

```
        r_reg<=r_next; // <= is non-blocking statement
```

```
    // next state logic [IMPORTANT]
```

```
    assign r_next = r_reg + 1;
```


```
    // output logic
```

```
    assign q=r_reg;
```

```
endmodule
```


Up/ down counter

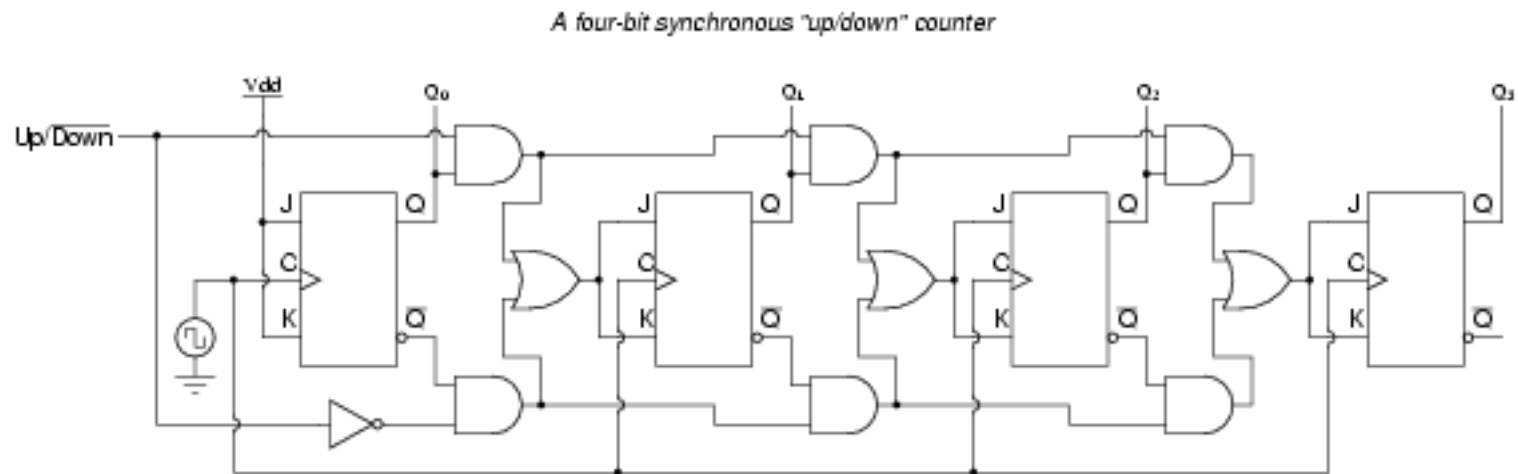- Design 8-bit synchronous up/down counter



8-bit up/down counter

module CounterUD

*(input wire clk,reset,ud,
output wire [7:0] q);*

// signal declaration

reg [7:0] r_reg;

wire [7:0] r_next;

// body, register

always @(posedge clk, posedge reset)

if (reset)

r_reg<=0;

else

r_reg<=r_next;

// next state logic [IMPORTANT]

assign r_next = (ud==1)?r_reg + 1:r_reg - 1;


// output logic

assign q=r_reg;

endmodule

Register

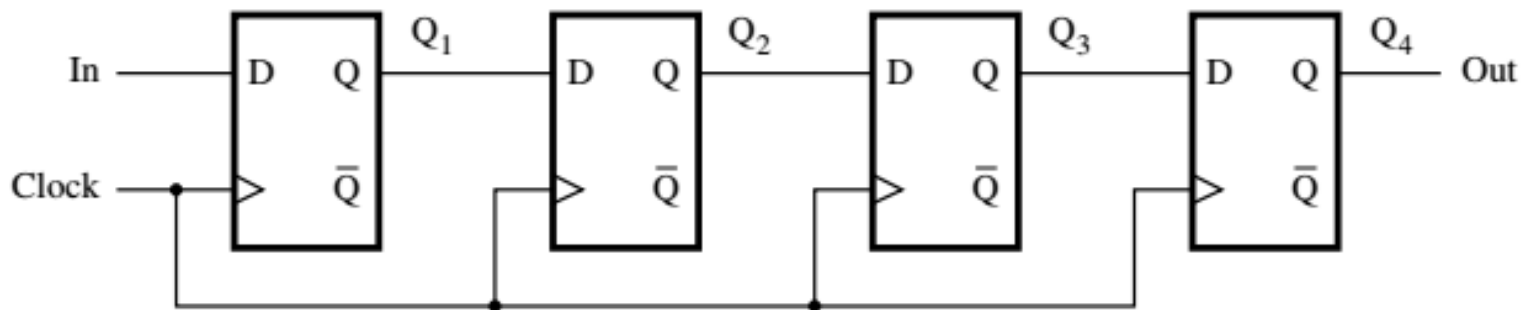- A register is a collection of D FFs that are controlled by the same clock and reset signals
- Serial In – Serial Out (SISO) shift register. The block diagram of 4-bit SISO shift register is shown in the following figure.



Register

- Sample code

```
module Shift_SISO


#(parameter N= 4) // 500,000,000 for 0.1Hz
    ( input wire clk,s_in,
      output wire      s_out    );
    // signal declaration
    reg [N-1:0] r_reg;
    wire [N-1:0] r_next;

    // body, register
    always @(posedge clk)
        r_reg<=r_next;

    // next state logic [IMPORTANT]
    assign r_next = {s_in,r_reg[N-1: 1]};

    // output logic
    assign s_out= r_reg[0];
endmodule
```

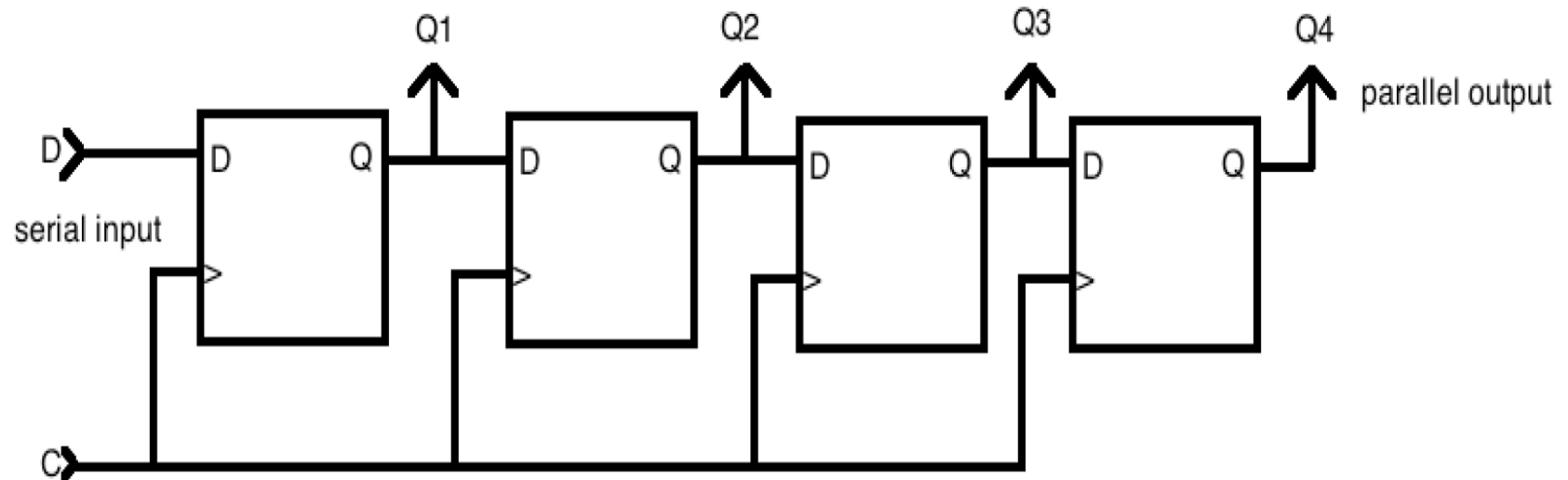Serial input – parallel output shift register



Register

- Sample code


```
module Shift_SIPO
(
    input wire clk,s_in,
    output wire [7:0] q_out );
    // signal declaration
    reg [7:0] r_reg;
    wire [7:0] r_next;

    // body, register
    always@(negedge clk)
        r_reg<=r_next;

    // next state logic [IMPORTANT]
    assign r_next = {s_in,r_reg[7:1]};

    // output logic
    assign q_out= r_reg;
```

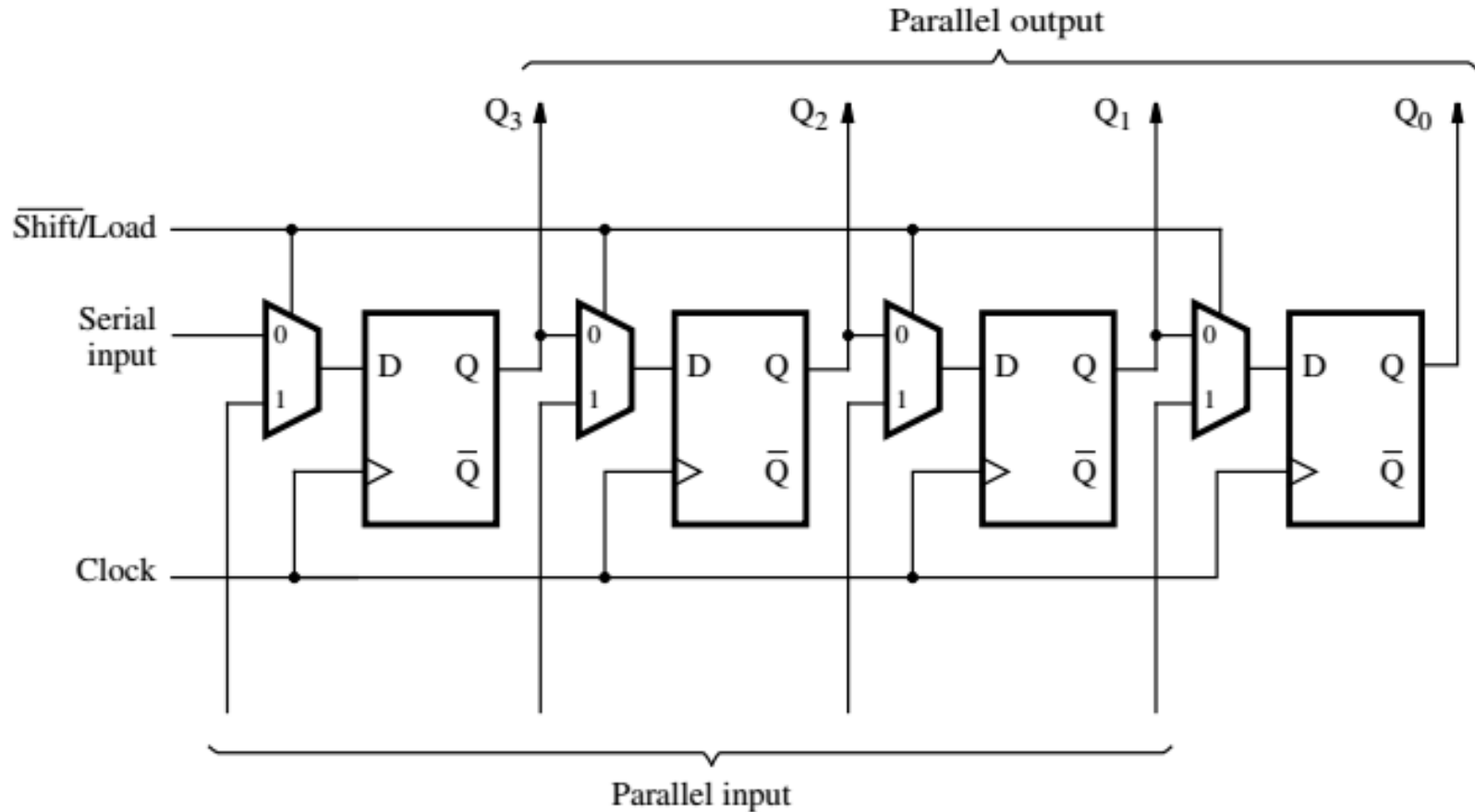Serial input – parallel output shift register



Synchronous sequential circuit

Finite state machine (FSM)

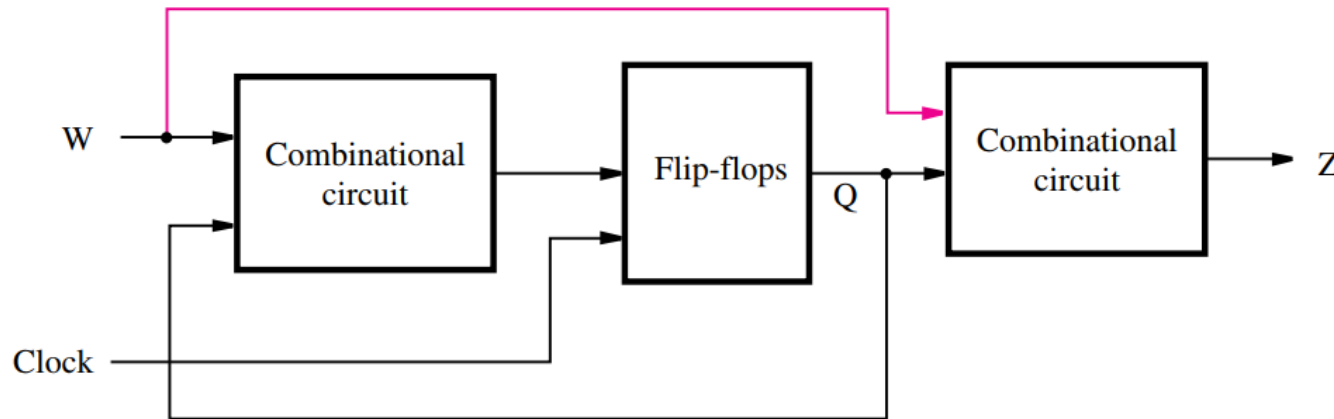


Figure 6.1 The general form of a sequential circuit.

- Synchronous sequential circuits are realized using combinational logic and one or more flip-flops.
- The circuit has a set of primary inputs, W , and produces a set of outputs, Z . The stored values in the flip-flops are referred to as the state, Q , of the circuit
- Under control of the clock signal, the flip-flops change their state as determined by the combinational logic that feeds the inputs of these flip-flops. the circuit moves from one state to another

Moore and Mealy type of FSM


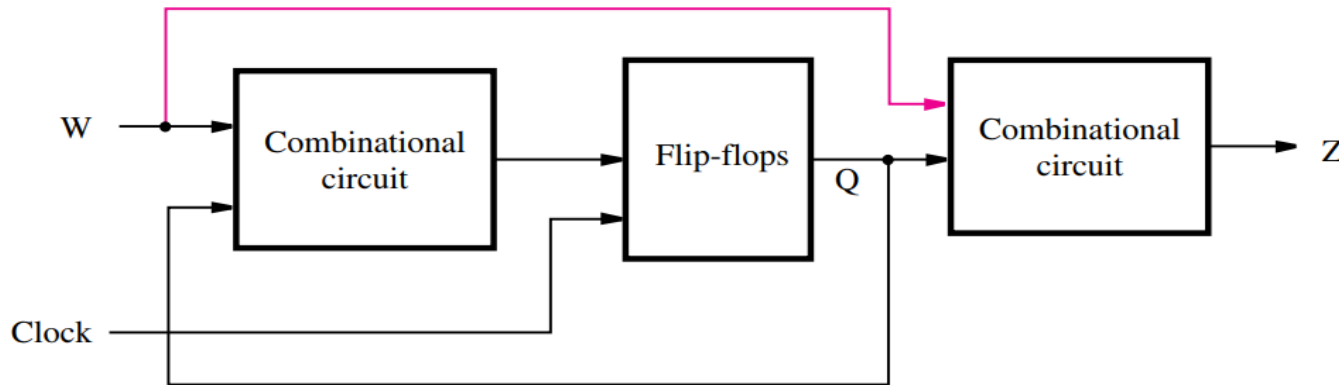


Figure 6.1 The general form of a sequential circuit.

- Mealy type: The outputs are a function of the present state of the flip-flops and of the primary inputs
- Moore type: The outputs always depend on the present state, they do not necessarily have to depend directly on the primary inputs
- that sequential circuits whose outputs depend only on the state of the circuit are of **Moore** type, while those whose outputs depend on both the state and the primary inputs are of **Mealy** type
- Sequential circuits are also called finite state machines (FSMs)

State Machine

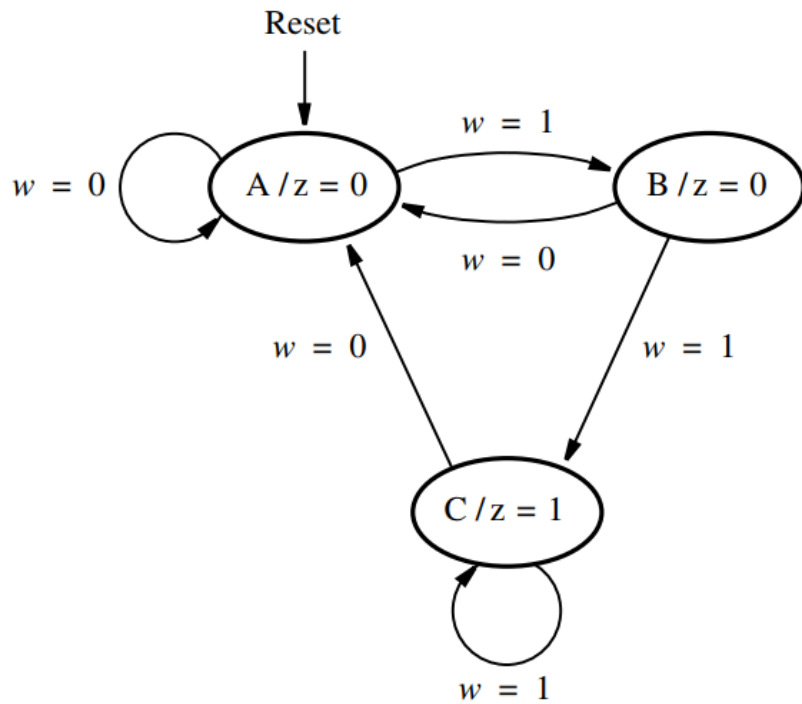- The first step in designing a finite state machine is to determine how many states are needed and which transitions are possible from one state to another



Present state	Next state		Output z
	w = 0	w = 1	
A	A	B	0
B	A	C	0
C	A	C	1


Figure 6.4 State table corresponding to Figure 6.3.

Figure 6.3 State diagram of a simple sequential circuit.

State Machine

```
module simple (Clock, Resetn, w, z);  
input Clock, Resetn, w; output z;  
reg [2:1] y, Y;  
parameter [2:1] A = 2'b00, B = 2'b01, C = 2'b10;  
// Define the next state combinational circuit  
always @(w, y)  
case (y)  
A: if (w) Y = B;  
else Y = A;  
B: if (w) Y = C;  
else Y = A;  
C: if (w) Y = C;  
else Y = A;  
default: Y = 2'bxx;  
endcase  
  
// Define the sequential block  
always @ (negedge Resetn, posedge Clock)  
if (Resetn == 0) y <= A;  
else y <= Y;  
// Define output  
assign z = (y == C);  
endmodule
```

FSM

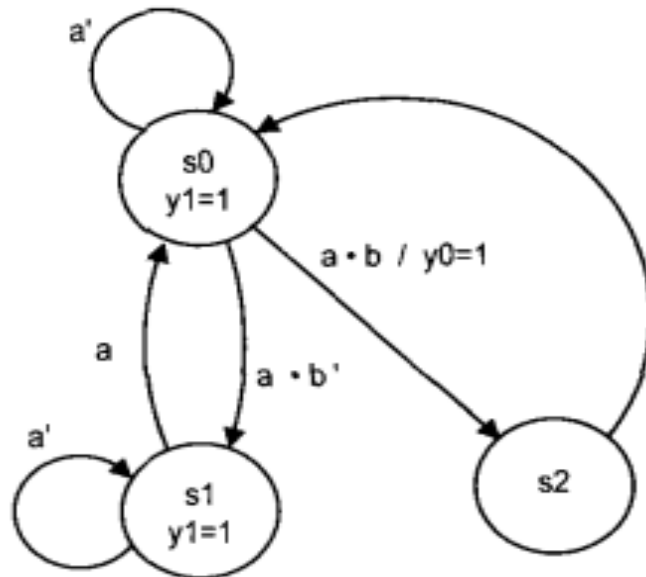

FSM

```
module fsm-eg-mult-seg
(
  input wire clk , reset ,
  input wire a , b ,
  output wire y0, y1 );
  //symbolic state declaration
  localparam [1:0] S0 = 2'b00; S1 = 2'b01
  , S2=2'b10;
  // signal declaration
  reg [1 : 0] state_reg,state_next ;

  // state register
  always @ (posedge clk ,posedge reset)
  if (reset)
    state_reg<=S0;
  else
    state_reg<=state_next;

  //next_state logic
  always @*
  case (state_reg)
```

```
    S0: if(a)
        if(b)
            state_next=S2;
        else
            state_next=S1;
        else
            state_next=S0;
    S1: if(a)
        state_next=S0;
        else
            state_next=S1;
    S2: state_next=S0;
  default: state_next=S0;
endcase

  //Moore outputlogic
  assign y1=(state_reg==S0)||(state_reg==S1);
  //Mealy outputlogic
  assign y0=(state_reg==S0)&a&b;
endmodule
```

Design of Counter Using Sequential Circuit

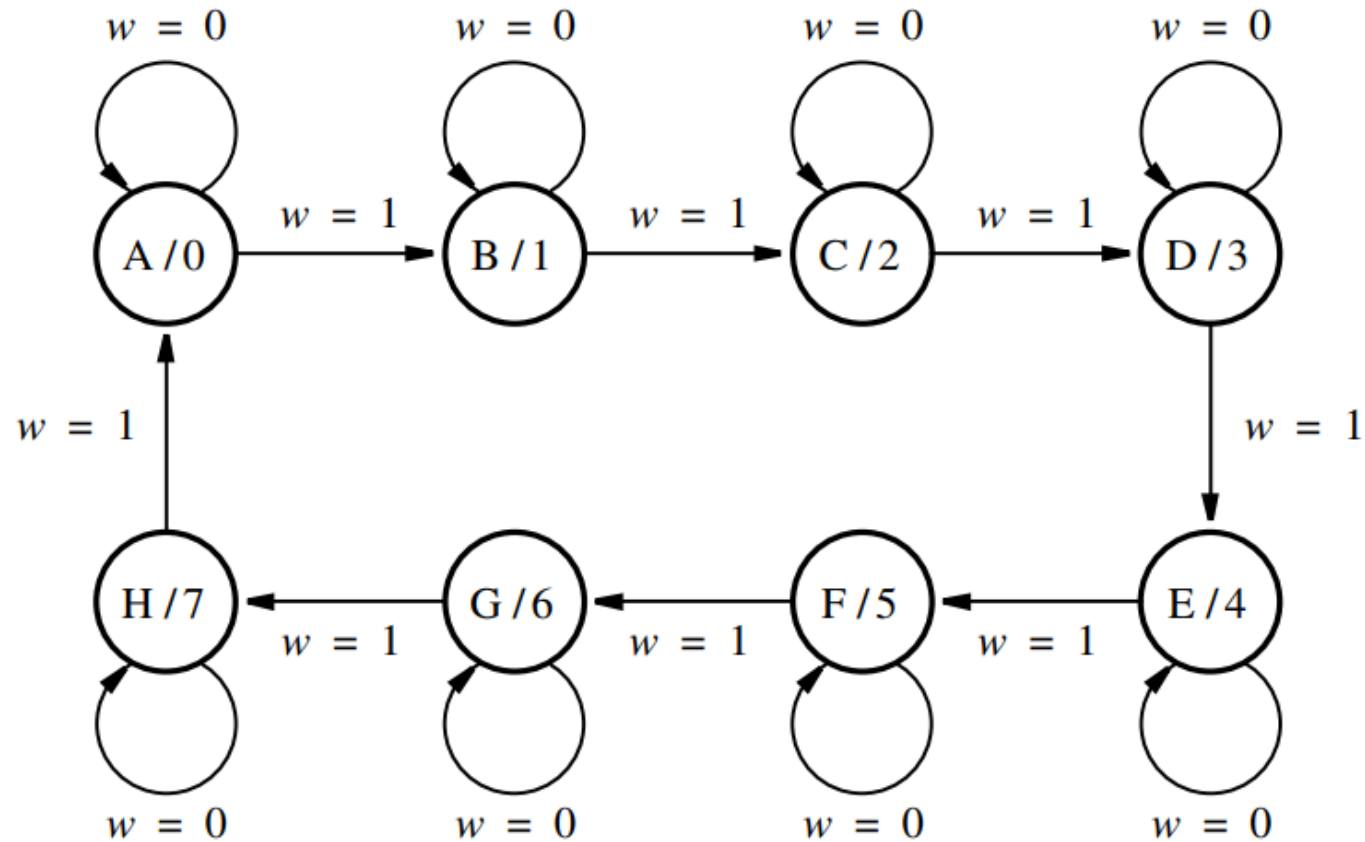


Figure 6.60 State diagram for the counter.

Design of Counter Using Sequential Circuit

Present state	Next state		Output
	$w = 0$	$w = 1$	
A	A	B	0
B	B	C	1
C	C	D	2
D	D	E	3
E	E	F	4
F	F	G	5
G	G	H	6
H	H	A	7

Figure 6.61 State table for the counter.

	Present state $y_2 y_1 y_0$	Next state		Count $z_2 z_1 z_0$
		$w = 0$	$w = 1$	
		$Y_2 Y_1 Y_0$	$Y_2 Y_1 Y_0$	
A	000	000	001	000
B	001	001	010	001
C	010	010	011	010
D	011	011	100	011
E	100	100	101	100
F	101	101	110	101
G	110	110	111	110
H	111	111	000	111

Figure 6.62 State-assigned table for the counter.

Design of Counter Using Sequential Circuit


- Sample code

Example

- A circuit must detect the sequence ...101... in a series data stream. The output stays at logic 1 until the sequence is detected again. The last 1 in one sequence may be the first 1 in the next, i.e. overlap must be catered for.


Input X 0 1 1 0 1 0 0 1 0 1 0 1 0 1 1

Output Z 0 0 0 0 1 1 1 1 1 1 0 0 1 1 0 0

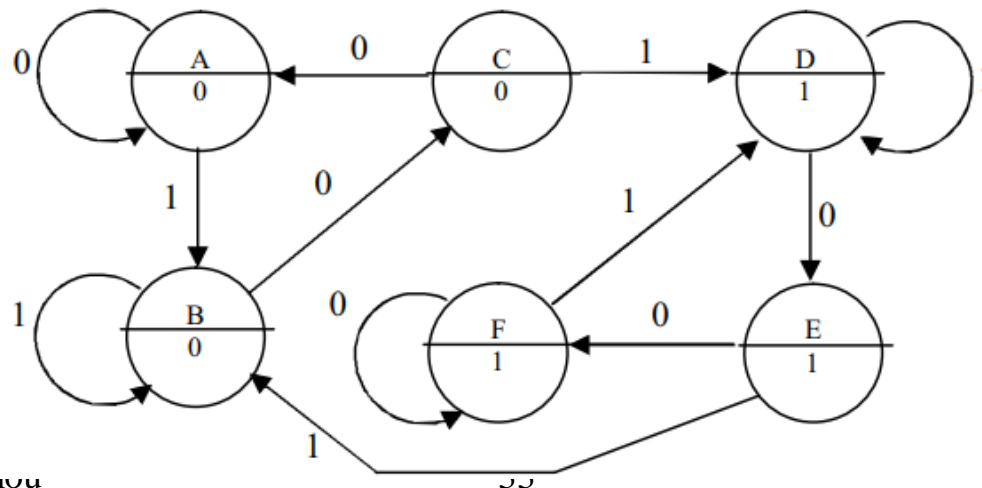

MẠCH CHIA XUNG (clock divider)

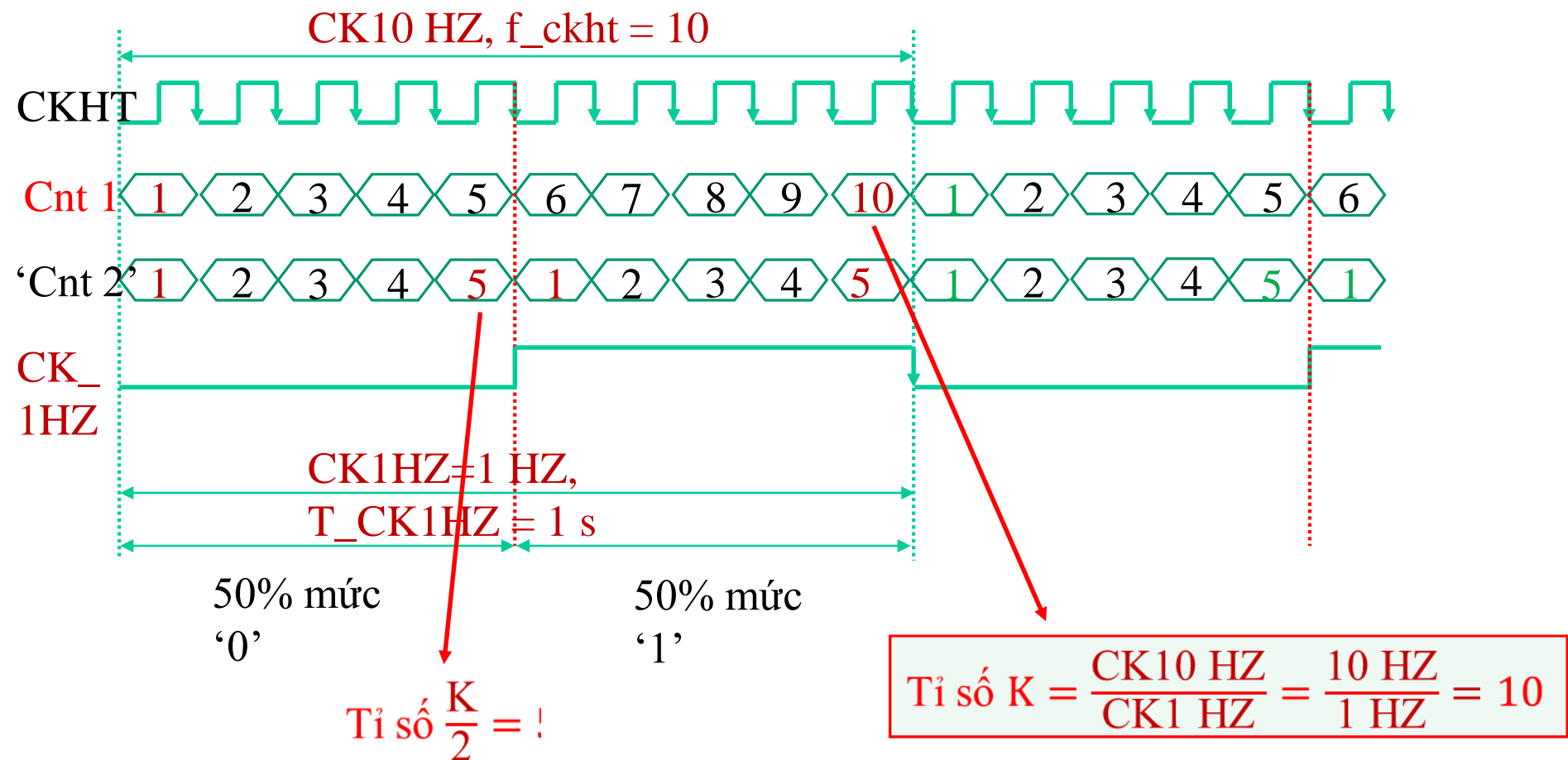- Thiết kế mạch chia tần số: chia xung đồng hồ hệ thống CLOCK để tạo xung 1 Hz (CK1HZ) có hệ số công tác 50%
 - Ckht hệ thống có chu kỳ T_{ckht} và tần số $f_{ckht} = N$
 - Clk_out có chu kỳ T_{clkout} và tần số $f_{clkout} = n$
 - Tỷ số $K = \frac{N}{n}$ (đếm từ 0 tới K-1 or 1 tới K)
 - So sánh kết quả mạch đếm với hằng số $\frac{K}{2}$ và đảo tín hiệu ngõ ra Clk_out



//TẠO XUNG 1 HZ TỪ XUNG HỆ THỐNG 50MHZ

module CK1HZ

#(parameter N= 26, M = 50 000 000)

(input wire clk, reset,
output wire q);

// signal declaration

reg [N-1:0] r_reg;

wire [N-1:0] r_next;

// body, register

always @(posedge clk, posedge reset)

if (reset)

r_reg <= 0;

else

r_reg <= r_next;

// next state logic

assign r_next = (r_reg == M)?0: r_reg + 1;

// output logic

assign q = (r_reg < M/2)?0:1; // ~q

endmodule


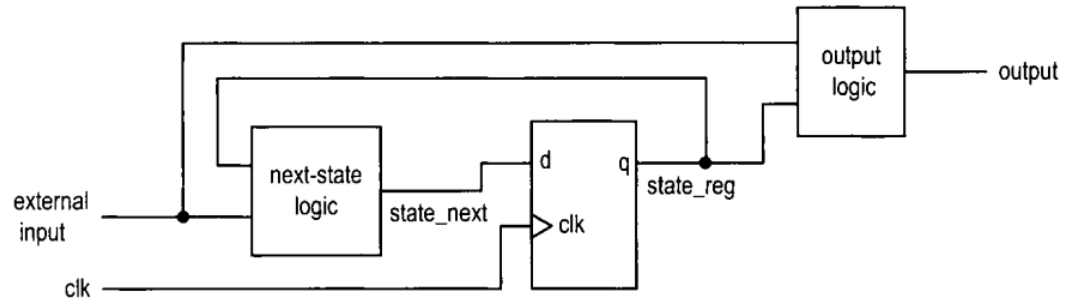


Figure 4.2 Block diagram of a synchronous system.

Homework #1

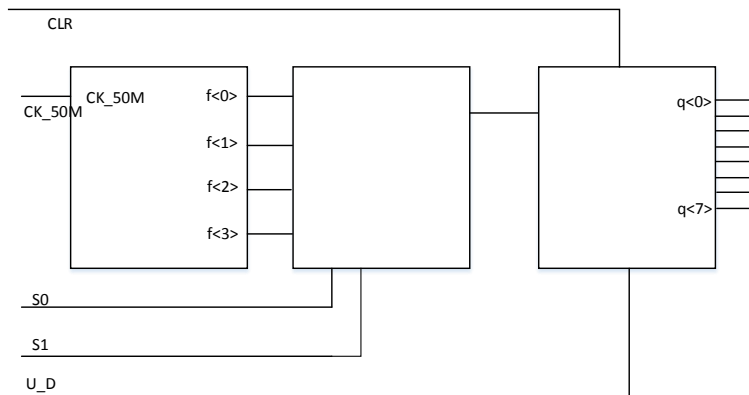
- Design the up/down counter. The input clock is 50Mhz. The circuit count up or down, with the frequency is selected by two switches ($f, 2*f, 4*f, 8*f$, where f is less than f_{clk}). The block diagram is shown as follows
- Pause: 0: stop counting, 1: count up/down
- Invert: invert the output.



Assignment #02

- Design a traffic light control circuit
- The input clock is 50Mhz

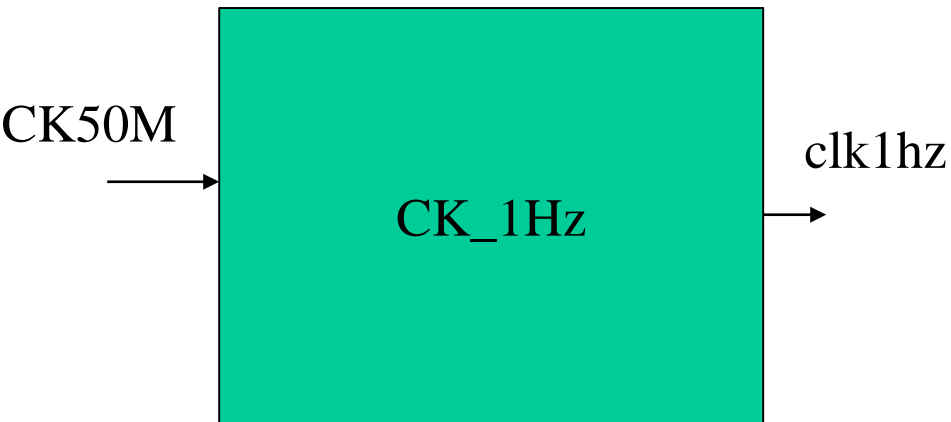1. Thiết kế mạch chia xung, tạo ra xung clock 1Hz từ clock hệ thống. Cho xung clock hệ thống 50MHz.




```
module CK_1HZ (clk50m, clk1hz);  
input clk50m;  
output reg clk1hz;  
  
reg [24:0] cnt;  
  
initial  
begin  
    cnt <= 1; clk1hz <= 0;  
end  
always @ (posedge clk50m)  
    if (cnt == 25 000 000)  
        clk1hz <= ~clk1hz;  
        cnt <= 1;  
    else    cnt <= cnt + 1;  
endmodule
```


2. Thiết kế mạch chia xung, tạo ra xung clock tùy ý từ clock hệ thống.

- Cho xung clock hệ thống 50MHz.
- Dùng tín hiệu ngõ vào MODE để chọn tần số ngõ ra


MODE	clk
0	1 Hz
1	2 Hz
2	10 Hz
3	50 Hz

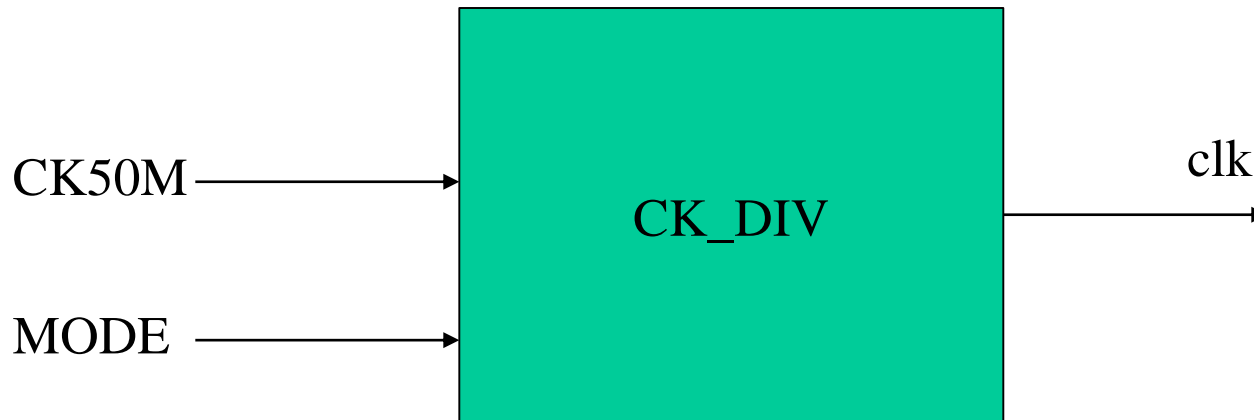

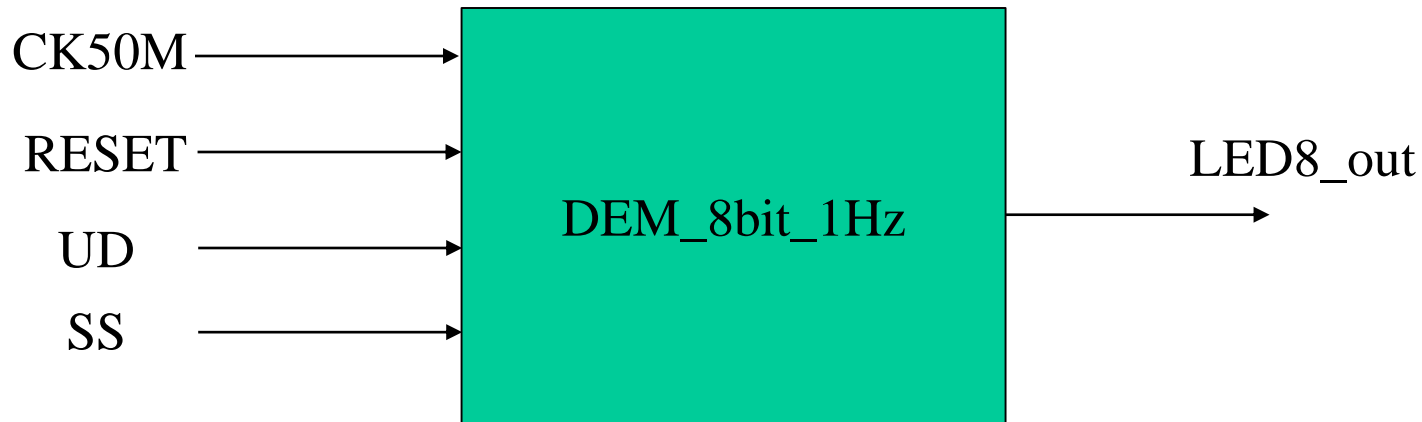3. Thiết kế mạch đếm lên/xuống hiển thị LED đơn như sau. Cho xung clock hệ thống 50MHz.



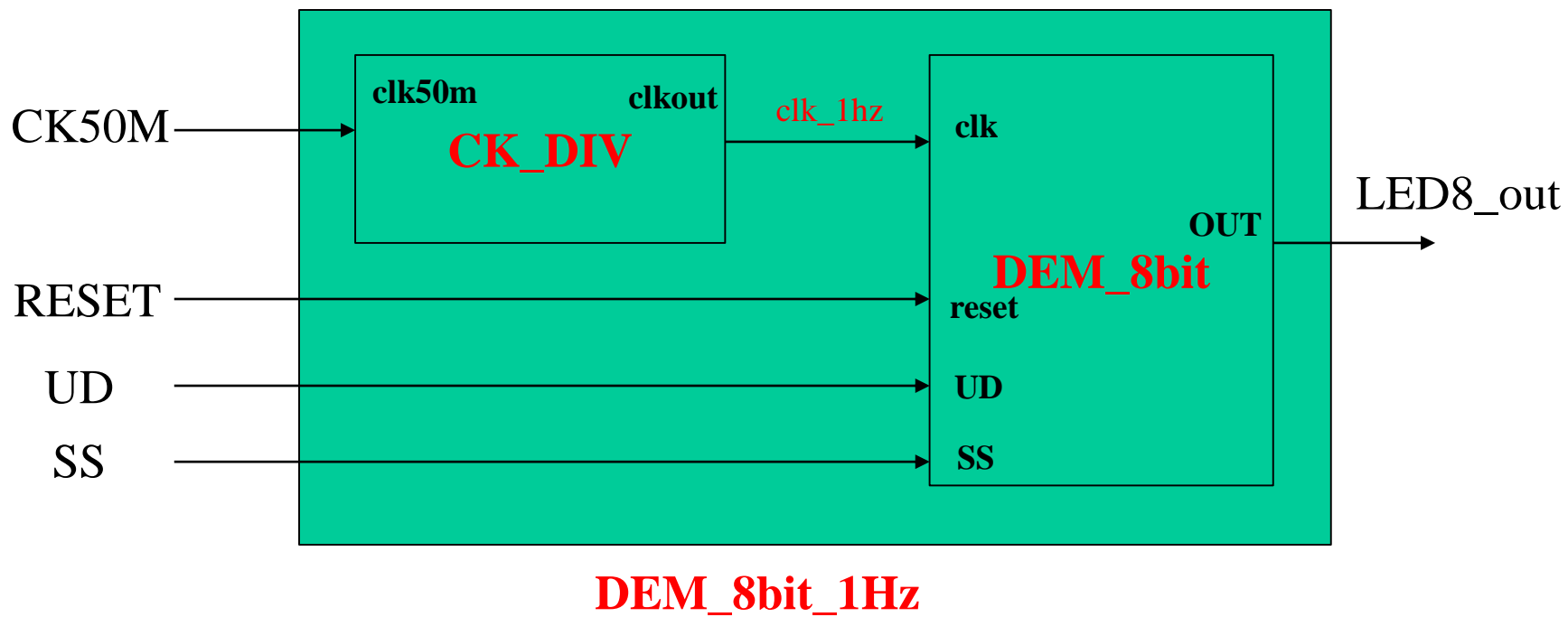- 8 LED hiển thị giá trị đếm lên/xuống theo xung 1Hz
- RESET mức '1'
- UD = 0: đếm lên, UD = 1: đếm xuống
- SS = 0: ngưng đếm, SS = 1: cho phép đếm



```
module CK_DIV (clk50m, clkout); → file CK_DIV.v
```

```
module DEM_8bit (clk, reset, UD, SS, LED8); → file DEM_8bit.v
```

```
    input clk, reset, UD, SS;
```

```
    output reg LED8_out;
```

```
    if (reset)
```

```
    else
```

```
        begin
```

```
        end
```

```
endmodule
```

```
module DEM_8bit_1Hz (clk, reset, UD, SS, LED8_out); → file DEM_8bit_1Hz.v
```

```
input clk, reset;          input UD, SS;
```


```
output [7:0] LED8_out;    wire clk_1hz;
```

```
CK_DIV IC1 (.clk50m(clk), .clkout(clk_1hz));
```

```
DEM_8bit IC2 (.clk(clk_1hz), .reset(reset), .UD(UD), .SS(SS), .OUT(LED8_out));
```


```
endmodule
```

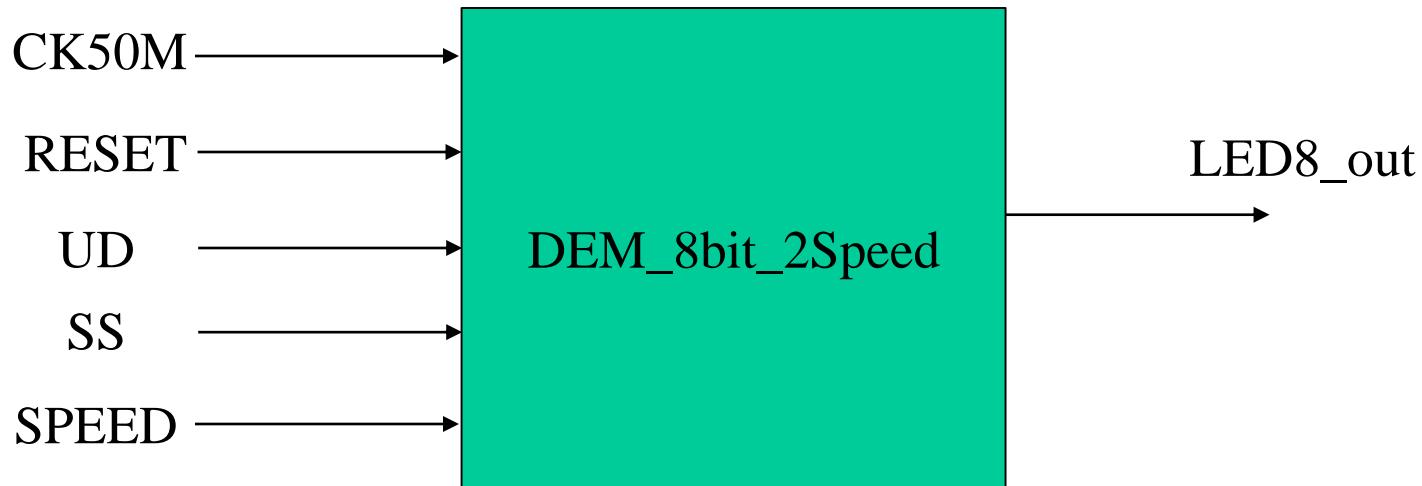4. Thiết kế mạch đếm lên/xuống hiển thị LED đơn như sau. Cho xung clock hệ thống 50MHz.




- 8 LED hiển thị giá trị đếm lên/xuống theo tốc độ tùy chọn bởi ngõ vào SPEED
- SPEED=0: 1Hz, SPEED=1: 2Hz
- RESET mức '1'
- UD = 0: đếm lên, UD = 1: đếm xuống
- SS = 0: ngưng đếm, SS = 1: cho phép đếm

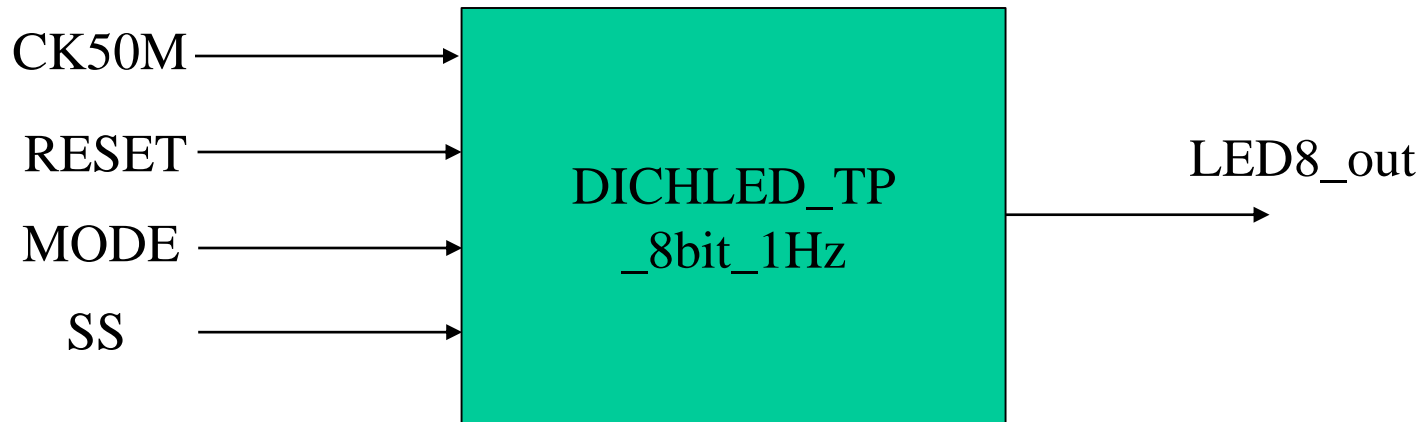5. Thiết kế mạch điều khiển 8 LED đơn như sau.
Cho xung clock hệ thống 50MHz.




- 8 LED dịch theo xung 1Hz
- RESET mức '1'
- MODE = 0: sáng dịch TSP, MODE = 1: sáng dịch PST
- SS = 0: ngưng dịch, SS = 1: cho phép dịch

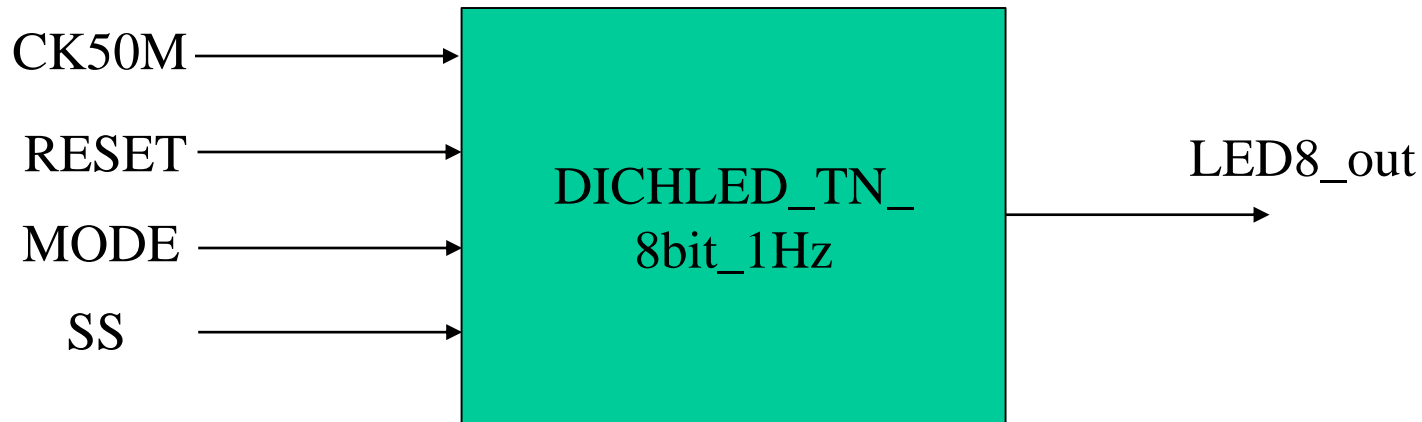6. Thiết kế mạch điều khiển 8 LED đơn như sau.
Cho xung clock hệ thống 50MHz.




- 8 LED dịch theo xung 1Hz
- RESET mức '1'
- MODE = 0: sáng dịch TTR, MODE = 1: sáng dịch TNV
- SS = 0: ngưng dịch, SS = 1: cho phép dịch

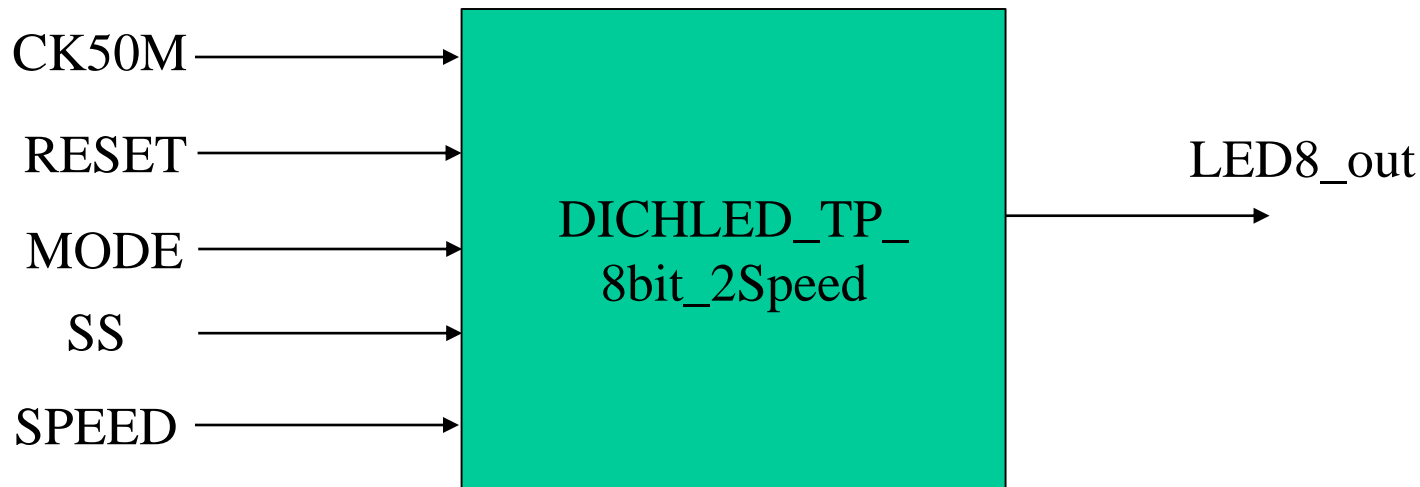7. Thiết kế mạch điều khiển 8 LED đơn như sau.
Cho xung clock hệ thống 50MHz.




- 8 LED hiển thị dịch LED theo tốc độ tùy chọn bởi ngõ vào SPEED
- SPEED=0: 1Hz, SPEED=1: 2Hz
- RESET mức '1'
- MODE = 0: sáng dịch TSP, MODE = 1: sáng dịch PST
- SS = 0: ngưng dịch, SS = 1: cho phép dịch

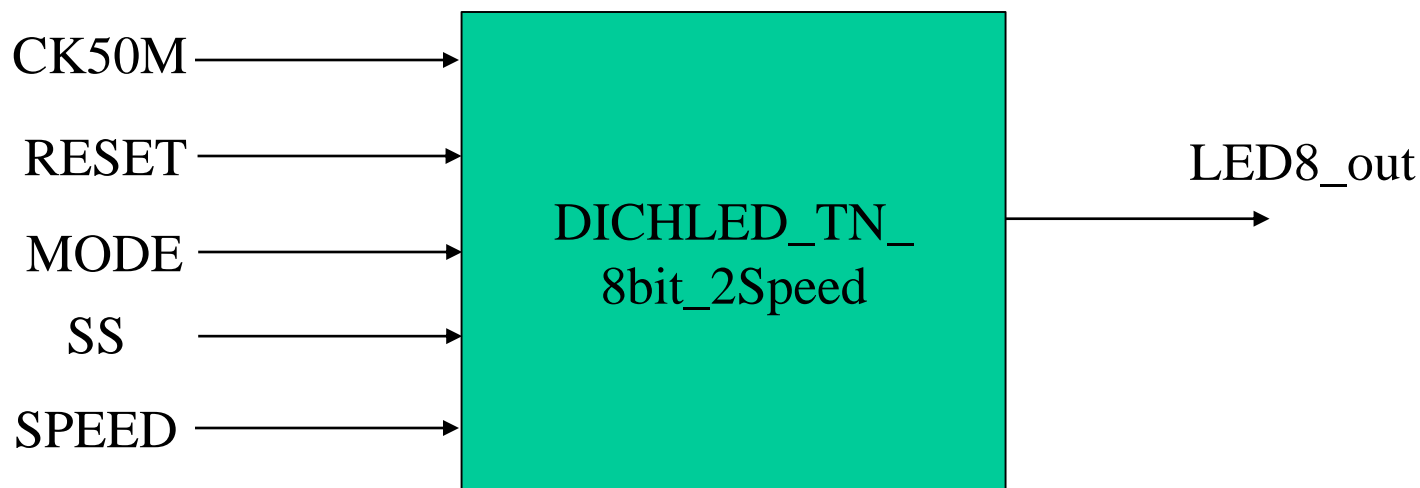8. Thiết kế mạch điều khiển 8 LED đơn như sau.
Cho xung clock hệ thống 50MHz.



- 8 LED hiển thị dịch LED theo tốc độ tùy chọn bởi ngõ vào SPEED
- SPEED=0: 1Hz, SPEED=1: 2Hz
- RESET mức '1'
- MODE = 0: sáng dịch TTR, MODE = 1: sáng dịch TNV
- SS = 0: ngưng dịch, SS = 1: cho phép dịch

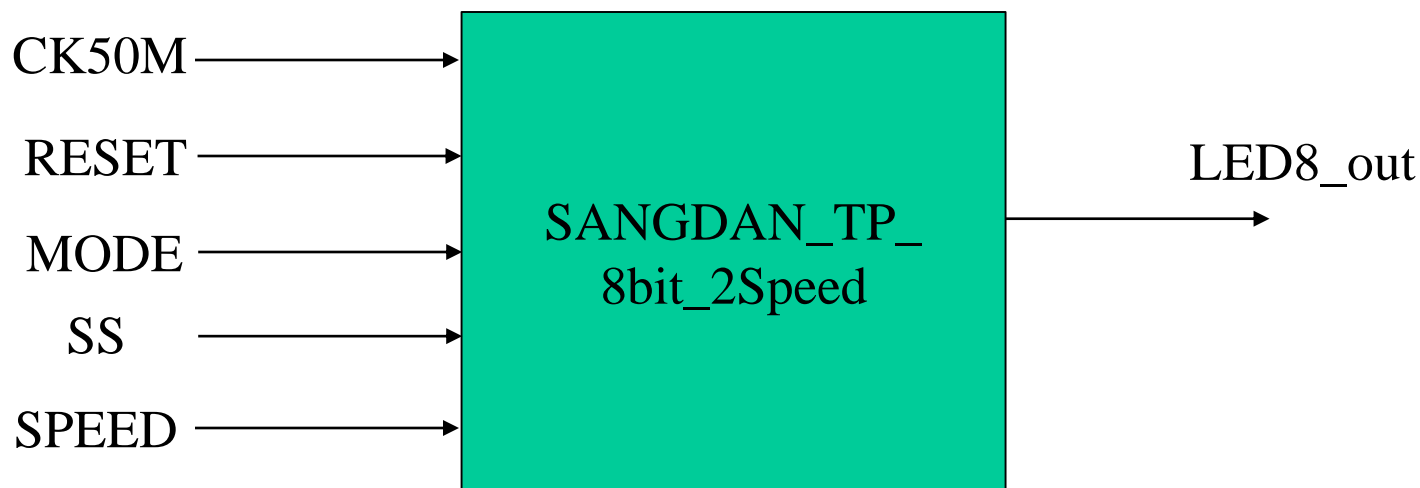9. Thiết kế mạch điều khiển 8 LED đơn như sau.
Cho xung clock hệ thống 50MHz.



- 8 LED hiển thị LED SÁNG DẦN theo tốc độ tùy chọn bởi ngõ vào SPEED
- SPEED=0: 1Hz, SPEED=1: 2Hz
- RESET mức '1'
- MODE = 0: sáng dần TSP, MODE = 1: sáng dần PST
- SS = 0: ngưng, SS = 1: cho phép

10. Thiết kế mạch điều khiển 8 LED đơn như sau.
Cho xung clock hệ thống 50MHz.



- 8 LED hiển thị LED SÁNG DẦN theo tốc độ tùy chọn bởi ngõ vào SPEED
- SPEED=0: 1Hz, SPEED=1: 2Hz
- RESET mức '1'
- MODE = 0: sáng dần TTR, MODE = 1: sáng dần TNV
- SS = 0: ngưng, SS = 1: cho phép

Ôn tập

- CK20M, CK50M, CK100M, ...
- Clock_out selection
- Điều khiển LED
 - Đếm lên/đếm xuống
 - Led sáng dịch:
 - TSP-PST
 - TTR-TNV
 - Led sáng dần
 - TSP-PST
 - TTR-TNV
- CMOS realization of logic gates

CMOS Realization of Logic Gates

- NOT
- 2-NAND, 3-NAND
- NOR
- OR
- 2-AND, 3-AND
- Schematic
- Truth table with explanation

