

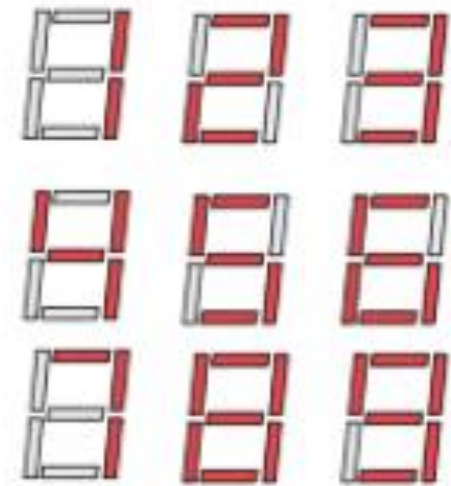


Counter with 7-seg display

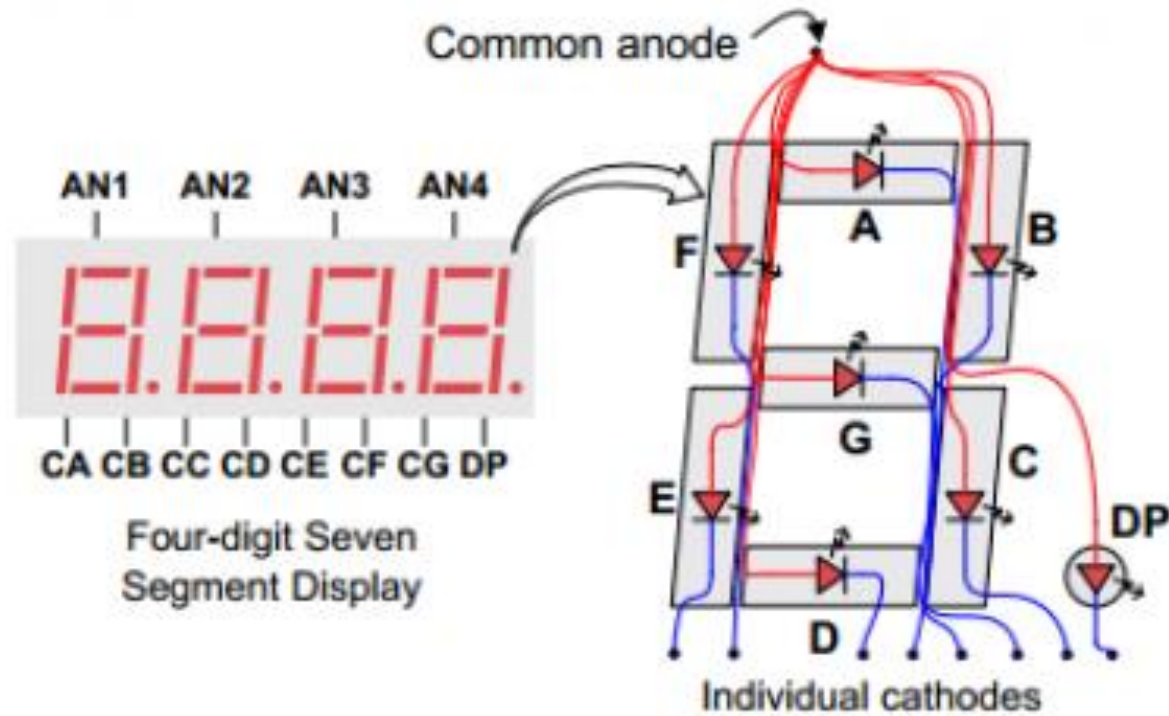

An un-illuminated seven-segment display, and nine illumination patterns corresponding to decimal digits


Figure 7. Seven-segment display

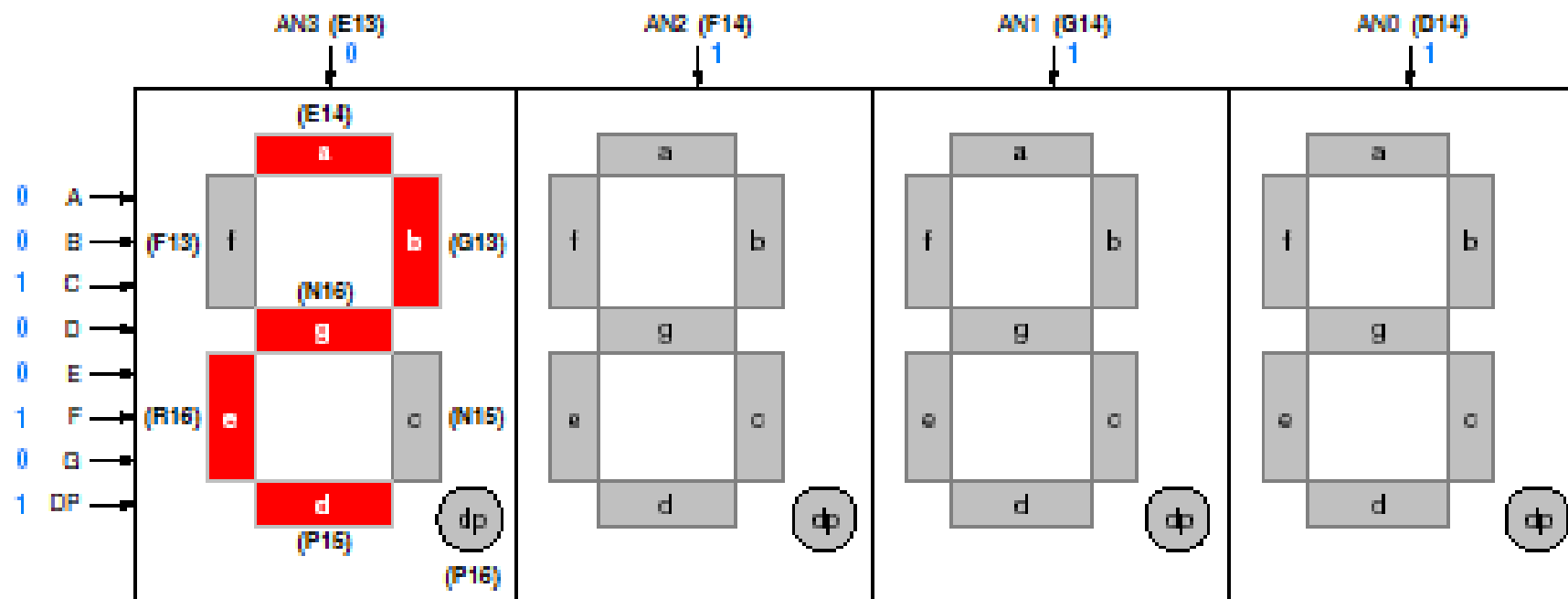

UG130_04_01_007034

Figure 3-1: Seven-Segment LED Digit Control

Hex to BCD

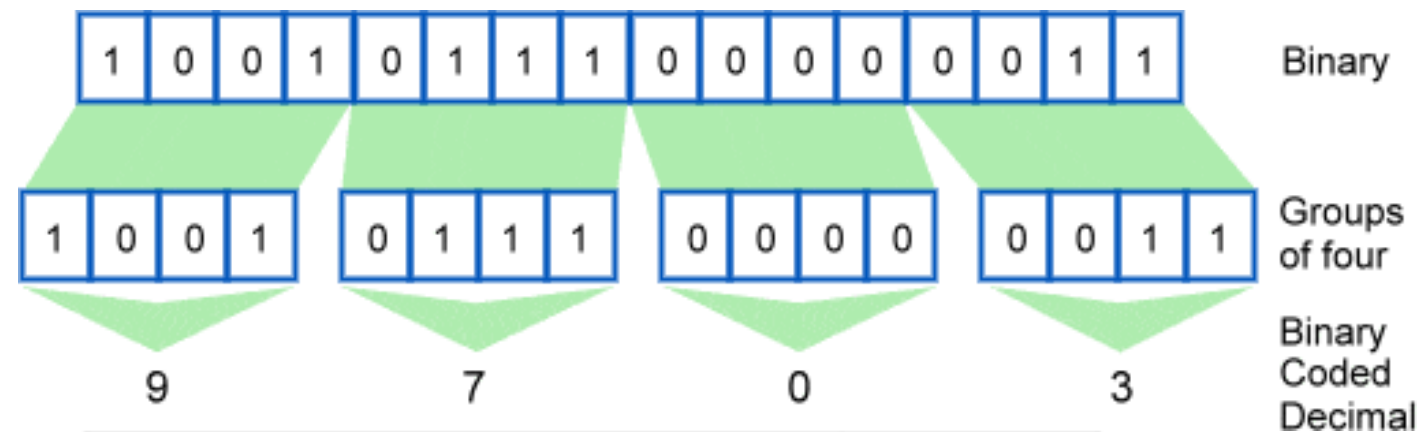

Operation	Tens	Units	Binary
HEX			E
Start			1 1 1 0
Shift 1		1	1 1 0
Shift 2		1 1	1 0
Shift 3		1 1 1	0
Add 3		1 0 1 0	0
Shift 4	1	0 1 0 0	
BCD	1	4	

1. Shift the binary number left one bit.
2. If 8 shifts have taken place, the BCD number is in the *Hundreds*, *Tens*, and *Units* column.
3. If the binary value in any of the BCD columns is 5 or greater, add 3 to that value in that BCD column.
4. Go to 1.


Operation	Hundreds	Tens	Units	Binary	
HEX				F	F
Start				1 1 1 1	1 1 1 1
Shift 1			1	1 1 1 1	1 1 1
Shift 2			1 1	1 1 1 1	1 1
Shift 3			1 1 1	1 1 1 1	1
Add 3			1 0 1 0	1 1 1 1	1
Shift 4		1	0 1 0 1	1 1 1 1	
Add 3		1	1 0 0 0	1 1 1 1	
Shift 5		1 1	0 0 0 1	1 1 1	
Shift 6		1 1 0	0 0 1 1	1 1	
Add 3		1 0 0 1	0 0 1 1	1 1	
Shift 7	1	0 0 1 0	0 1 1 1	1	
Add 3	1	0 0 1 0	1 0 1 0	1	
Shift 8	1 0	0 1 0 1	0 1 0 1		
BCD	2	5	5		

```
module add3(in,out);  
input [3:0] in;  
output [3:0] out;  
reg [3:0] out;  
  
always @ (in)  
    case (in)  
        4'b0000: out <= 4'b0000;  
        4'b0001: out <= 4'b0001;  
        4'b0010: out <= 4'b0010;  
        4'b0011: out <= 4'b0011;  
        4'b0100: out <= 4'b0100;  
        4'b0101: out <= 4'b1000;  
        4'b0110: out <= 4'b1001;  
        4'b0111: out <= 4'b1010;  
        4'b1000: out <= 4'b1011;  
        4'b1001: out <= 4'b1100;  
        default: out <= 4'b0000;  
    endcase  
endmodule
```


Here is a structural Verilog module corresponding to the logic diagram.

```
module binary_to_BCD(A,ONES,TENS,HUNDREDS);
input [7:0] A;
output [3:0] ONES, TENS;
output [1:0] HUNDREDS;
wire [3:0] c1,c2,c3,c4,c5,c6,c7;
wire [3:0] d1,d2,d3,d4,d5,d6,d7;


assign d1 = {1'b0,A[7:5]};
assign d2 = {c1[2:0],A[4]};
assign d3 = {c2[2:0],A[3]};
assign d4 = {c3[2:0],A[2]};
assign d5 = {c4[2:0],A[1]};
assign d6 = {1'b0,c1[3],c2[3],c3[3]};
assign d7 = {c6[2:0],c4[3]};
add3 m1(d1,c1);
add3 m2(d2,c2);
add3 m3(d3,c3);
add3 m4(d4,c4);
add3 m5(d5,c5);
add3 m6(d6,c6);
add3 m7(d7,c7);
assign ONES = {c5[2:0],A[0]};
assign TENS = {c7[2:0],c5[3]};
assign HUNDREDS = {c6[3],c7[3]};
```

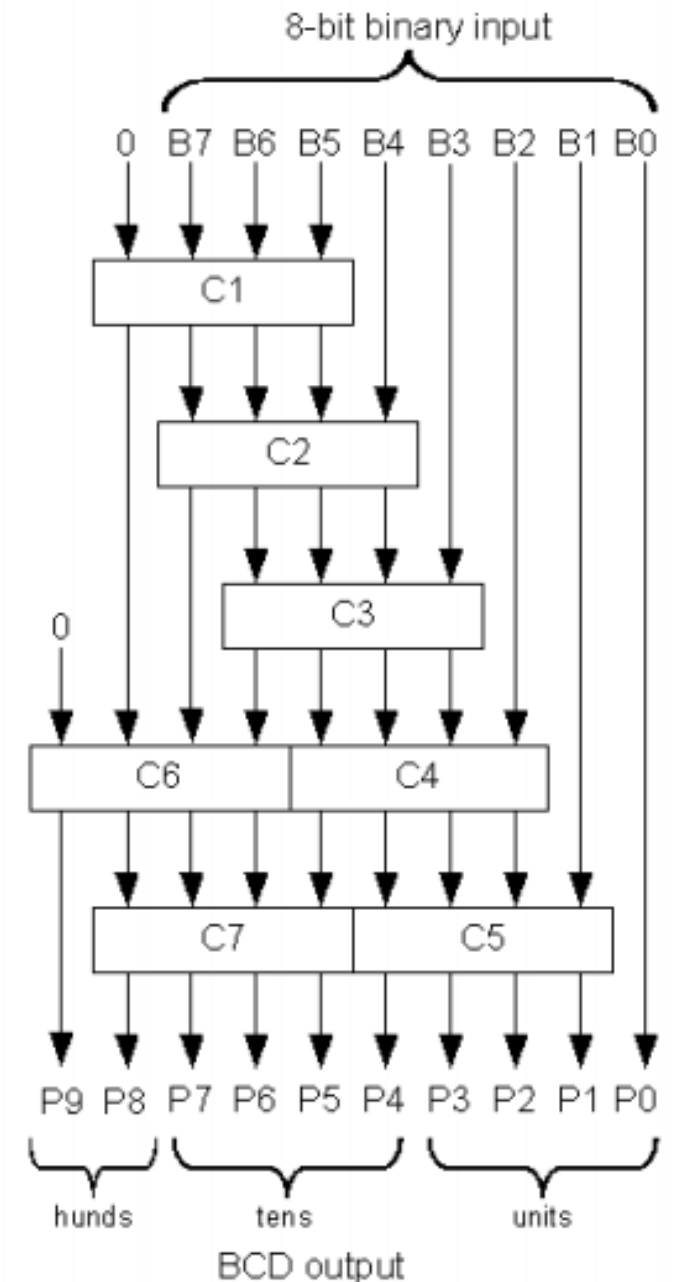

Time multiplexing module

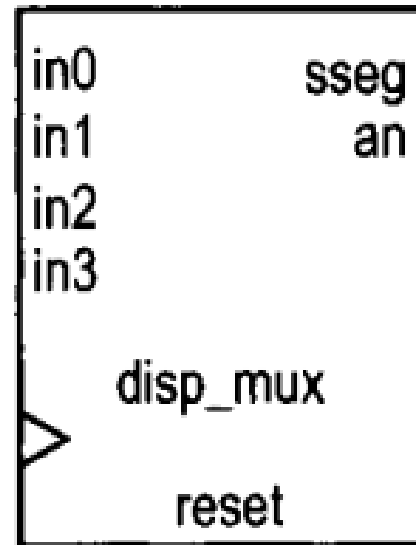

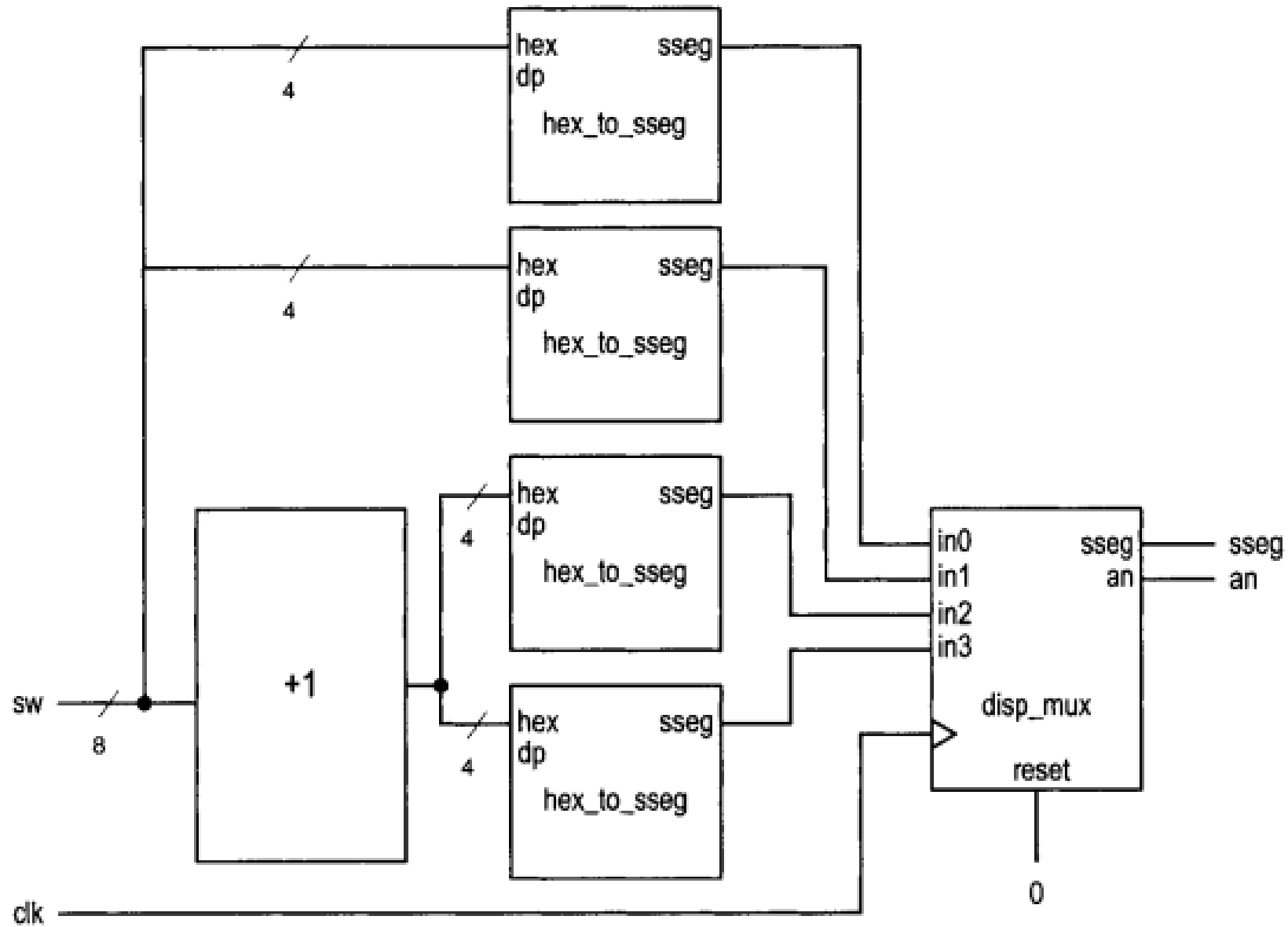(a) Block diagram of an LED time-multiplexing module



(b) Block diagram of a decoder testing circuit

Numbers	Common Cathode		Common Anode	
	(DP)GFEDCBA	HEX Code	(DP)GFEDCBA	HEX Code
0	00111111	0x3F	11000000	0xC0
1	00000110	0x06	11111001	0xF9
2	01011011	0x5B	10100100	0xA4
3	01001111	0x4F	10110000	0xB0
4	01100110	0x66	10011001	0x99
5	01101101	0x6D	10010010	0x92
6	011111101	0x7D	10000010	0x82
7	00000111	0x07	11111000	0xF8
8	01111111	0x7F	10000000	0x80
9	01101111	0x6F	10010000	0x90

Multiplexing 7-seg display

