

Chapter 5: Sequential Circuits

Do Duy Tan, Ph.D


Email: tandd@hcmute.edu.vn

<https://sites.google.com/site/tandduy/>

Department of Computer and Communication Engineering
Faculty of Electrical and Electronics Engineering, HCMUTE

Original slides composed by **Dr. Truong Ngoc Son** – Modified by **Dr. Do Duy Tan**
Department of Computer and Communication Engineering


RS Latch

 

(a) Circuit

Clk	S	R	$Q(t + 1)$
0	x	x	$Q(t)$ (no change)
1	0	0	$Q(t)$ (no change)
1	0	1	0
1	1	0	1
1	1	1	x

(b) Characteristic table

 


RS Latch

- Verilog HDL

```
module RS_LATCH(  
input wire R,S,CLK,  
output reg Q,Qb  
);  
always @(R,S,CLK) begin  
if/*((CLK==1)&&(S==0)&&(R==1))*/*({CLK,S,R}  
==3'b101) begin Q=0;Qb=1;end  
else if ((CLK==1)&&(S==1)&&(R==0)) begin  
Q=1;Qb=0;end  
end  
endmodule
```

JK Flip Flop

 


Input					Output	
Pre	CLR	CLK	J	K	Q	QD
0	0	x	x	x	1	1
0	1	x	x	x	1	0
1	0	x	x	x	0	1
1	1	0	x	x	Q ₀	QD ₀
1	1	↓	0	0	Q ₀	QD ₀
1	1	↓	0	1	0	1
1	1	↓	1	0	1	0
1	1	↓	1	1	NOT Q	NOT QD

JK Flip Flop

- Verilog HDL


D Latch

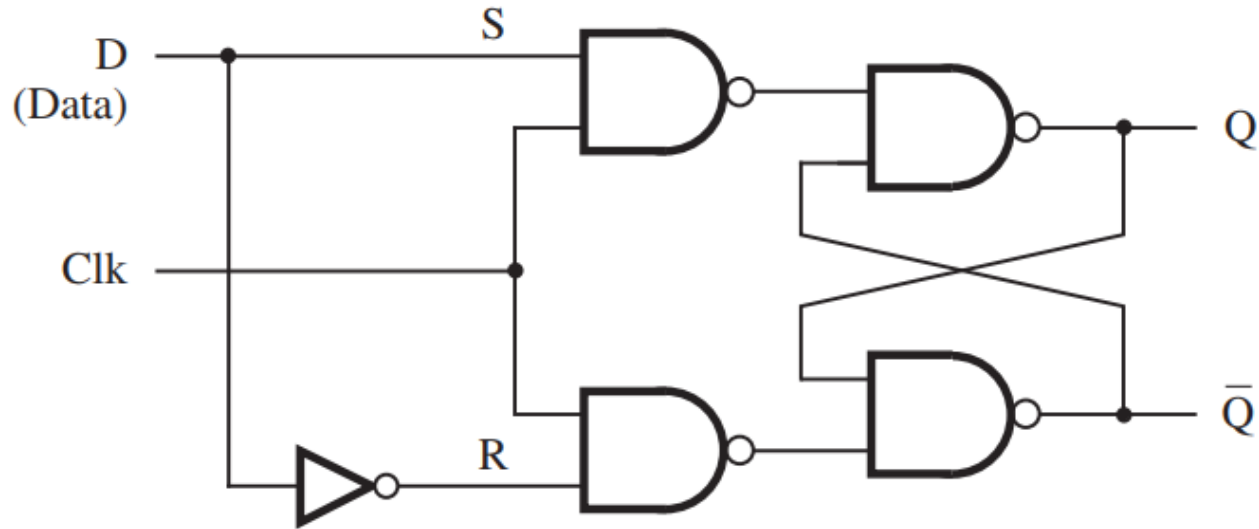

(a) Circuit

Clk	D	$Q(t + 1)$
0	x	$Q(t)$
1	0	0
1	1	1

(b) Characteristic table

 

(c) Graphical symbol

D Latch

- Verilog HDL


```
module D_latch (D, Clk, Q);  
  input D, Clk;  
  output reg Q;
```

```
  always @(D, Clk)  
    if (Clk)  
      Q = D;
```

LATCH

```
endmodule
```

D Flip-Flop

 

P-SET	CLR	D	CLK	Q_{n+1}	
0	1	X	X	1	(preset)
1	0	X	X	0	(clear)
0	0	X	X	?	(illegal)
1	1	0	↓	0	
1	1	1	↓	1	

D Flip-Flop

- The difference between a latch and a flip-flop is
 - A latch is asynchronous, and the outputs can change as soon as the inputs do (or at least after a small propagation delay)
 - A flip-flop is edge-triggered and only changes state when a control signal goes from high to low or low to high

```
module flipflop (D, Clock, Q);  
    input D, Clock;  
    output reg Q;
```

FLIP-FLOP

```
    always @(posedge Clock)  
        Q = D;
```


```
endmodule
```

Latches vs. Flip-Flops

Flip-Flop

```
module flipflop
(
  input clk,
  input d,
  output reg q
);

 
always @(posedge clk)
begin
  q <= d;
end
endmodule
```




Latch

```
module latch
(
  input clk,
  input d,
  output reg q
);

 always @(clk or d)
begin
  if ( clk )
    q <= d;
end
endmodule
```




T Flip-Flop

 


(a) Circuit

T	$Q(t+1)$
0	$Q(t)$
1	$\bar{Q}(t)$

(b) Characteristic table

 

(c) Graphical symbol

 


(d) Timing diagram

T Flip-Flop

```
module T_FF(  
    input wire t, clk,  
    output reg q, qb );  
  
initial  
begin  
    q=1 ;  
    qb=0;  
end  
  
always @( posedge clk)  
    if (t) begin  
        q = ~q ;  
        qb = !qb;  
    end  
endmodule
```


Shift Register

 

(a) Circuit

Clock Pulse No	QA	QB	QC	QD
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	0	1
5	0	0	0	0

	In	Q ₁	Q ₂	Q ₃	Q ₄ = Out
t_0	1	0	0	0	0
t_1	0	1	0	0	0
t_2	1	0	1	0	0
t_3	1	1	0	1	0
t_4	1	1	1	0	1
t_5	0	1	1	1	0
t_6	0	0	1	1	1
t_7	0	0	0	1	1

 

Shift Register

- Instance shift register using D-FF.

```
module DFF(  
input wire d,clk,  
output reg q );  
always @(posedge clk)  
q = d ;  
endmodule  
  
// Serial input - serial output using DFF  
module SISO(  
input wire in, clk,  
output wire out) ;  
// signal declaration  
wire q1,q2,q3 ;  
//module instance  
DFF ff1 (in,clk,q1);  
DFF ff2 (q1,clk,q2);  
DFF ff3 (q2,clk,q3);  
DFF ff4 (q3,clk,out);  
endmodule
```

Module instance review

- Modules can be instantiated from within other modules. When a module is instantiated, connections to the ports of the module must be specified.
- There are two ways to make port connections.
 - Connection by name, in which variables connected to each of module inputs or outputs are specified in a set of parenthesis following the name of the ports. In this method order of connections is not significant.
 - Ordered connection. In this method the order of the ports must match the order appearing in the instantiated module.


Module instance review

- Connection by name

```
module dff (  
  input wire clk, d,  
  output reg q );  
  always @(posedge clk) q = d;  
endmodule
```

```
module top (  
  input wire d_in, clk,  
  output wire q_out);
```
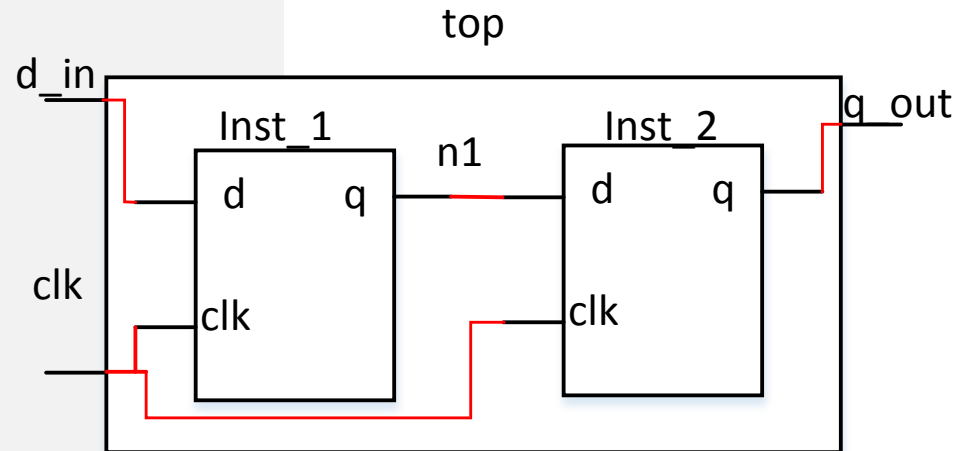
```
  wire n1;  
  dff Inst_1 (.d(d_in), .q(n1), .clk(clk));  
  dff Inst_2 (.clk(clk), .d(n1), .q(q_out));  
endmodule
```




Module instance review

- Connection by order

```
module dff (  
  input wire clk, d,  
  output reg q );  
  always @(posedge clk) q = d;  
endmodule
```


```
module top (  
  input wire d_in, clk,  
  output wire q_out);  
  wire n1;
```
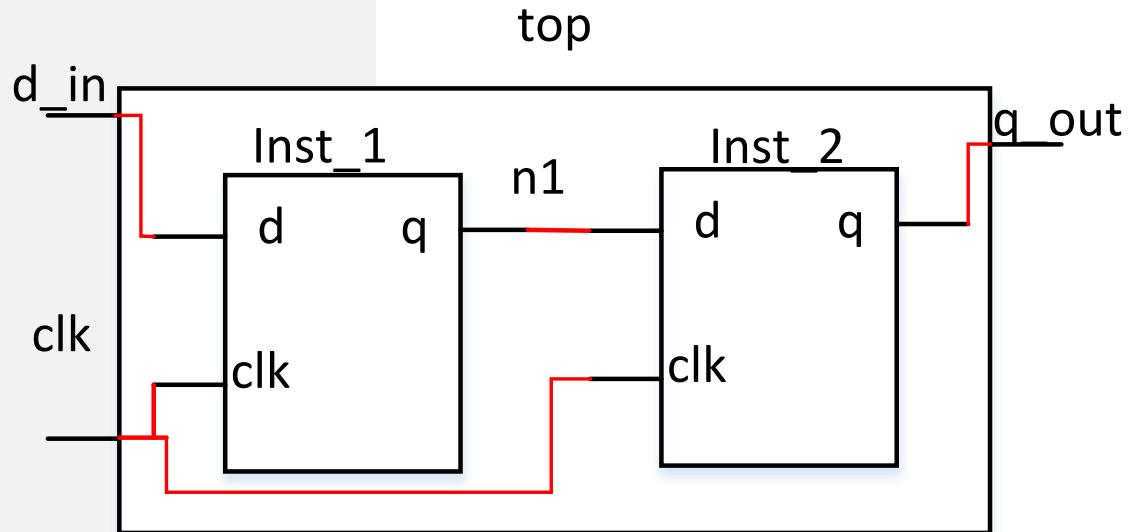
```
  dff Inst_1 (clk, d_in, n1);  
  dff Inst_2 (clk, n1, q_out);  
endmodule
```




Example - Ripple Adder

```
module FullAdder(a, b, ci, r, co);  
    input a, b, ci;  
    output r, co;  
  
    assign r = a ^ b ^ ci;  
    assign co = a&ci | a&b | b&cin;  
  
endmodule
```

 

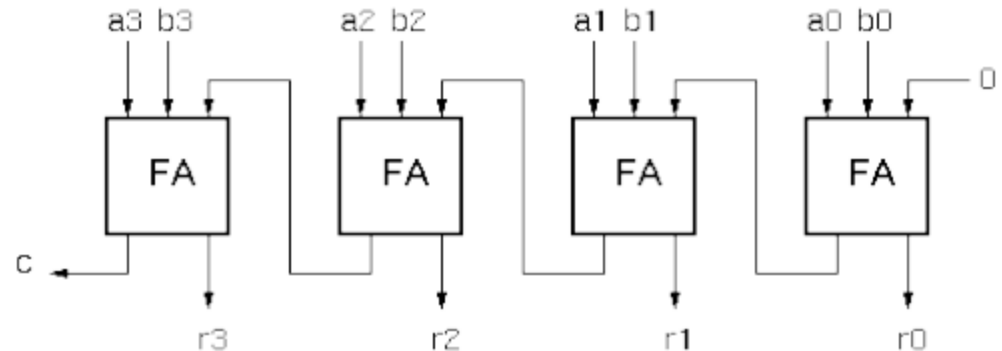
```
module Adder(A, B, R);  
    input [3:0] A;  
    input [3:0] B;  
    output [4:0] R;
```



```
    wire c1, c2, c3;  
    FullAdder  
    add0(.a(A[0]), .b(B[0]), .ci(1'b0), .co(c1), .r(R[0]) ),  
    add1(.a(A[1]), .b(B[1]), .ci(c1), .co(c2), .r(R[1]) ),  
    add2(.a(A[2]), .b(B[2]), .ci(c2), .co(c3), .r(R[2]) ),  
    add3(.a(A[3]), .b(B[3]), .ci(c3), .co(R[4]), .r(R[3]) );  
endmodule
```

Shift Register – Serial input, parallel outputs

- Instance the shift register using D-FF

 


Shift Register – Serial input parallel outputs

```
module DFF(  
  input wire d,clk,  
  output reg q );  
  always @(posedge clk)  
    q = d ;  
endmodule  
  
// Serial input - parallel output using DFF  
module SIPO(  
  input wire in, clk,  
  output wire [3:0] q) ;  
  // signal declaration  
  
  //module instance  
  DFF ff1 (in,clk,q[0]);  
  DFF ff2 (q[0],clk,q[1]);  
  DFF ff3 (q[1],clk,q[2]);  
  DFF ff4 (q[2],clk,q[3]);  
endmodule
```

Counter

A simultaneous "up" and "down" counter

 


Clock cycle	Q ₂	Q ₁	Q ₀
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0

Q₁ changes


Q₂ changes

Combinational circuit

Asynchronous Counter (not same clock)

 

(a) Circuit

 


(b) Timing diagram


Counter

- Instance counter with T-FF

Synchronous counter (same clock source)

 

(a) Circuit

 

(b) Timing diagram

Figure 5.21 A four-bit synchronous up-counter.

Counter

- Instance counter with T-FF

Example - Ripple Adder Generator

Parameters give us a way to generalize our designs. A module becomes a “generator” for different variations. Enables design/module reuse. Can simplify testing.

Declare a parameter with default value.

```
module Adder(A, B, R);
```

```
parameter N = 4;
```

Note: this is not a port. Acts like a “synthesis-time” constant.

```
input [N-1:0] A;
```

```
input [N-1:0] B;
```

Replace all occurrences of “4” with “N”.

```
output [N:0] R;
```

```
wire [N:0] C;
```

variable exists only in the specification - not in the final circuit.

```
genvar i;
```

Keyword that denotes synthesis-time operations

```
generate
```

For-loop creates instances (with unique names)

```
for (i=0; i<N; i=i+1) begin:bit
```

```
FullAdder add(.a(A[i], .b(B[i]), .ci(C[i]), .co(C[i+1]), .r(R[i]));
```

```
end
```

```
endgenerate
```

```
assign C[0] = 1'b0;
```

```
assign R[N] = C[N];
```

```
endmodule
```

```
Adder adder4 ( ... );
```

```
Adder #(.N(64))
```


```
adder64 ( ... );
```

*Overwrite parameter
N at instantiation.*

Homework

- Design a circuit to control 4 LEDs
 - Light LEDS sequentially from (1) **left to right** then (2) turn 8 LEDs off sequentially from left to right (one-by-one).
 - The frequency is adjusted by two switches
 - The input clock is 50Mhz

 - Left-to-right
- Right-to-left
- Center-to-2side
- 2side-to-center



LED_SANG_DICH_TSP (input clk, input reset, output reg [7:0] LED)

clk	state	LED[7]	LED[6]	LED[5]	LED[4]	LED[3]	LED[2]	LED[1]	LED[0]
posedge	1	1	0	0	0	0	0	0	0
posedge	2	0	1	0	0	0	0	0	0
posedge	3	0	0	1	0	0	0	0	0
posedge	4	0	0	0	1	0	0	0	0
posedge	5	0	0	0	0	1	0	0	0
posedge	6	0	0	0	0	0	1	0	0
posedge	7	0	0	0	0	0	0	1	0
posedge	8	0	0	0	0	0	0	0	1
posedge	9	0	0	0	0	0	0	0	0
posedge	1	1	0	0	0	0	0	0	0

(a) Sau đó tắt hết

(b) sau đó tắt hết và lặp lại

```
module DICH8LED_TSP(clk, reset, LED8);  
input clk, reset;  
output reg [7:0] LED8;  
  
always @(posedge clk)  
    if(reset)  
        LED8 = 8'b1000_0000;  
    else  
        LED8 = LED8 >> 1;  
endmodule
```

```

module DICH8LED_TSP_REPEAT(clk, reset,
LED8);
input clk, reset;
output reg [7:0] LED8;
always @(posedge clk)
    if (reset)
        LED8 = 8'b1000_0000;
    else
        if (LED8 == 8'b0000_0000)
            LED8 = 8'b1000_0000;
        else LED8 = LED8 >> 1;
endmodule

```

LED_SANG_DICH_PST (input clk, input reset, output reg [7:0] LED)

clk	state	LED[7]	LED[6]	LED[5]	LED[4]	LED[3]	LED[2]	LED[1]	LED[0]
posedge	1	0	0	0	0	0	0	0	1
posedge	2	0	0	0	0	0	0	1	0
posedge	3	0	0	0	0	0	1	0	0
posedge	4	0	0	0	0	1	0	0	0
posedge	5	0	0	0	1	0	0	0	0
posedge	6	0	0	1	0	0	0	0	0
posedge	7	0	1	0	0	0	0	0	0
posedge	8	1	0	0	0	0	0	0	0
posedge	9	0	0	0	0	0	0	0	0
posedge	1	0	0	0	0	0	0	0	1

(a) Sau đó tắt hết

(b) sau đó tắt hết và lặp lại

LED_SANG_DICH_TTR (input clk, input reset, output reg [7:0] LED)

clk	state	LED[7]	LED[6]	LED[5]	LED[4]	LED[3]	LED[2]	LED[1]	LED[0]
posedge	1	0	0	0	1	1	0	0	0
posedge	2	0	0	1	0	0	1	0	0
posedge	3	0	1	0	0	0	0	1	0
posedge	4	1	0	0	0	0	0	0	1
posedge	5	0	0	0	0	0	0	0	0
posedge	1	0	0	0	1	1	0	0	0

(a) Sau đó tắt hết

(b) sau đó tắt hết và lặp lại


```
module DICH8LED_TTR(clk, reset, LED8);  
input clk, reset;  
output reg [7:0] LED8;  
  
always @(posedge clk)  
    if(reset)  
        LED8 = 8'b0001_1000;  
    else  
        LED8[7:4] = LED8[7:4] << 1;  
        LED8[3:0] = LED8[3:0] >> 1;  
endmodule
```

```

module DICH8LED_TTR_REPEAT(clk, reset, LED8);
input clk, reset;
output reg [7:0] LED8;
always @(posedge clk)
    if (reset)
        LED8 = 8'b0001_1000;
    else if (LED8==8'b0000_0000)
        LED8 = 8'b0001_1000;
    else
        LED8[7:4] = LED8[7:4] << 1;
        LED8[3:0] = LED8[3:0] >> 1;
endmodule

```

LED_SANG_DICH_TNV (input clk, input reset, output reg [7:0] LED)

clk	state	LED[7]	LED[6]	LED[5]	LED[4]	LED[3]	LED[2]	LED[1]	LED[0]
posedge	1	1	0	0	0	0	0	0	1
posedge	2	0	1	0	0	0	0	1	0
posedge	3	0	0	1	0	0	1	0	0
posedge	4	0	0	0	1	1	0	0	0
posedge	5	0	0	0	0	0	0	0	0
posedge	1	0	0	0	0	0	0	0	0

(a) Sau đó tắt hết

(b) sau đó tắt hết và lặp lại

LED_SANG_DAN_TSP (input clk, input reset, output reg [7:0] LED)

clk	state	LED[7]	LED[6]	LED[5]	LED[4]	LED[3]	LED[2]	LED[1]	LED[0]
posedge	1	1	0	0	0	0	0	0	0
posedge	2	1	1	0	0	0	0	0	0
posedge	3	1	1	1	0	0	0	0	0
posedge	4	1	1	1	1	0	0	0	0
posedge	5	1	1	1	1	1	0	0	0
posedge	6	1	1	1	1	1	1	0	0
posedge	7	1	1	1	1	1	1	1	0
posedge	8	1	1	1	1	1	1	1	1
posedge	9	0	0	0	0	0	0	0	0
posedge	1	1	0	0	0	0	0	0	0

(a) Sau đó tắt hết

(b) sau đó tắt hết và lặp lại

```
module SANGDAN_8LED_TSP(clk, reset, LED8);  
input clk, reset;  
output reg [7:0] LED8;  
always @(posedge clk)  
    if(reset)  
        LED8 = 8'b1000_0000;  
    else if (LED8==8'hFF)  
        LED8 = 8'b0000_0000;  
    else if (LED8!=8'h00)  
        LED8 = LED8 >> 1; LED8[7] = 1'b1;  
        // LED8 = LED8 | LED8>>1;  
        // LED8 = 8'b10000000 + LED8>>1;  
endmodule
```

```

module SANGDAN_8LED_TSP_REPEAT(clk, reset,
LED8);
input clk, reset;
output reg [7:0] LED8;
always @(posedge clk)
    if(reset)
        LED8 = 8'b1000_0000;
    else if (LED8==8'hFF)
        LED8 = 8'b0000_0000;
    else
        LED8 = LED8 >> 1;
        LED8[7] = 1'b1;
endmodule

```

LED_SANG_DAN_PST (input clk, input reset, output reg [7:0] LED)

clk	state	LED[7]	LED[6]	LED[5]	LED[4]	LED[3]	LED[2]	LED[1]	LED[0]
posedge	1	0	0	0	0	0	0	0	1
posedge	2	0	0	0	0	0	0	1	1
posedge	3	0	0	0	0	0	1	1	1
posedge	4	0	0	0	0	1	1	1	1
posedge	5	0	0	0	1	1	1	1	1
posedge	6	0	0	1	1	1	1	1	1
posedge	7	0	1	1	1	1	1	1	1
posedge	8	1	1	1	1	1	1	1	1
posedge	9	0	0	0	0	0	0	0	0
posedge	1	0	0	0	0	0	0	0	1

(a) Sau đó tắt hết

(b) sau đó tắt hết và lặp lại

LED_SANG_DICH_TSP_PST (input clk, input reset, input SS, input MODE, output reg [7:0] LED)

clk	state	LED[7]	LED[6]	LED[5]	LED[4]	LED[3]	LED[2]	LED[1]	LED[0]
posedge	1	1	0	0	0	0	0	0	0
posedge	2	0	1	0	0	0	0	0	0
posedge	3	0	0	1	0	0	0	0	0
posedge	4	0	0	0	1	0	0	0	0
posedge	5	0	0	0	0	1	0	0	0
posedge	6	0	0	0	0	0	1	0	0
posedge	7	0	0	0	0	0	0	1	0
posedge	8	0	0	0	0	0	0	0	1
posedge	9	0	0	0	0	0	0	0	0
posedge	1	1	0	0	0	0	0	0	0

(a) Sau đó tắt hết

(b) sau đó tắt hết và lặp lại

LED_SANG_DICH_TSP_PST (input clk, input reset, input SS, input
MODE, output reg [7:0] LED)

always @ (posedge clk)

if (reset) out = 8'b0000_0000;

else

 if (SS==1)

 if (MODE==0) //TSP

 if (out==8'b0000_0000)

 out=8'b1000_0000;

 else out=out>>1;

 else //MODE==1 //PST

 if (out==8'b0000_0000)

 out=8'b0000_0001;

 else out=out<<1;

 else out = out;

endmodule

LED_SANG_DICH_TTR_TNV (input clk, input reset, input SS, input
MODE, output reg [7:0] LED)

always @ (posedge clk)

if (reset) out = 8'b0000_0000;

else

 if (SS==1)

 if (MODE==0) % TTR

 if (out==8'b0000_0000)

 out=8'b0001_1000;

 else out[7:4]=out[7:4]<< 1;

 out[3:0]=out[3:0]>> 1;

 else //MODE==1 % TNV

 if (out==8'b0000_0000)

 out=8'b1000_0001;

 else out[7:4]=out[7:4]>> 1;

 out[3:0]=out[3:0]<<1;

end

endmodule

LED_SANG_DAN_TSP_PST (input clk, input reset, input SS, input MODE,
output reg [7:0] LED)

always @ (posedge clk)

if (reset) out = 8'b0000_0000;

else

 if (SS==1)

 if (MODE==0) //TSP

 if (out==8'b1111_1111)

 out=8'b0000_0000;

 else if (out== 8'b0000_0000)

 out= 8'b1000_0000;

 else out=out>>1 + 8'b1000_0000;

 else //MODE==1 //PST

 if (out==8'b1111_1111)

 out=8'b0000_0000;

 else if (out== 8'b0000_0000)

 out= 8'b0000_0001;

 else out=out<<1 + 8'b0000_0001;

 else out = out;

endmodule